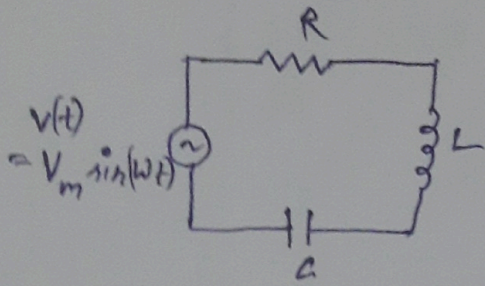


L-C-R circuit

(1)



Impedance

$$Z = \sqrt{R^2 + (X_C - X_L)^2}$$

$$X_C = \frac{1}{\omega C}$$

↳ Capacitive Reactance


$$X_L = \omega L$$

↳ Inductive Reactance

$$I(t) = I_m \sin(\omega t + \phi)$$

$$I_m = \frac{V_m}{Z}$$

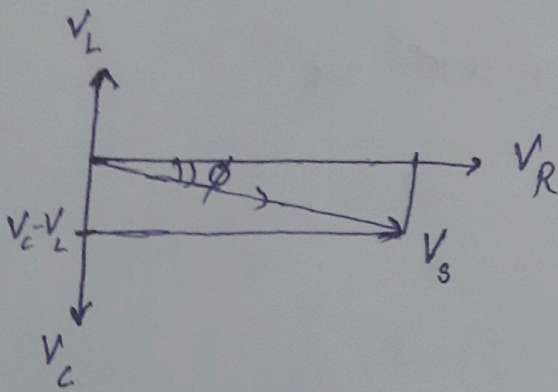↳ phase by which current leads the voltage



$\phi \Rightarrow$ angle by which supply voltage lags the current

\therefore circuit is capacitive in nature.

Example

100 μ F capacitor in series with a 40 Ω resistance, connected to a 110 V (rms) / 60 Hz supply.

What is time lag between current max & voltage max?

$$60 \text{ Hz} \rightarrow \omega = 2\pi \times 60 \approx 377 \text{ rad/s}$$

Capacitive reactance

$$\frac{1}{\omega C} = \frac{1}{377 \times 10^{-4}} \approx 26.5 \Omega$$

$$Z = \sqrt{40^2 + (26.5)^2} \approx 48 \Omega$$

$$I_{\text{rms}} = \frac{110}{48} = 2.29 \text{ A} \Rightarrow I_m = 2.29 \sqrt{2}$$

$$I_m = 3.24 \text{ A}$$

Angle by which ~~the~~ current leads voltage

$$\phi = \tan^{-1} \frac{X_C}{R} \approx 0.56 \text{ rad}$$

Time lags b/w current & voltage max.

(2)

$$\frac{\phi}{\omega} = 1.55 \text{ ms}$$

$$f = 1 \text{ kHz} \rightarrow \omega = 6283 \text{ rad/sec}$$

$$\omega C = 6283 \times 10^{-4} = 0.63 \Omega^{-1}$$

$$X_c = \frac{1}{\omega C} = 1.59 \Omega$$

$$Z = \sqrt{40^2 + (1.59)^2} = 40.03 \Omega$$

$$\frac{X_c}{R} = \frac{1.59}{40} = 0.0397 \Rightarrow \phi = \tan^{-1} \left(\frac{X_c}{R} \right) \approx 0.039 \text{ rad}$$

$$\text{Time lag} = \frac{0.039}{6283} = 6.3 \times 10^{-6} \text{ sec}$$

Analytical solution:

(3)

$$L \frac{dI}{dt} + IR + \frac{Q}{C} = V_m \sin \omega t$$

$$I = \frac{dQ}{dt}$$

$$L \frac{d^2 I}{dt^2} + R \frac{dI}{dt} + \frac{1}{C} \cdot I = V_m \omega \cos(\omega t)$$

$$I = I_m \sin(\omega t + \phi)$$

$$\frac{dI}{dt} = I_m \omega \cos(\omega t + \phi)$$

$$\frac{d^2 I}{dt^2} = -I_m \omega^2 \sin(\omega t + \phi)$$

$$I_m \omega \left[\underbrace{\left(-L\omega + \frac{1}{\omega C} \right)}_{X_C - X_L} \sin(\omega t + \phi) + R \cos(\omega t + \phi) \right] = V_m \omega \cos \omega t$$

$$I_m \omega \cancel{C}$$

$$R = A \cos \theta$$

$$X_C - X_L = A \sin \theta$$

$$A^2 = R^2 + (X_C - X_L)^2 = Z^2 \Rightarrow A = Z$$

$$\tan \theta = \frac{X_C - X_L}{R}$$

$$I_m Z \cos(\omega t + \phi - \theta) = V_m \cos(\omega t)$$

$$I_m Z = V_m \Rightarrow I_m = \frac{V_m}{Z}$$

$$\theta = \phi$$

$$I = \frac{V_m}{Z} \sin(\omega t + \phi) ; \tan \phi = \frac{X_C - X_L}{R}$$

Resonance

(4)

$$I_m = \frac{V_m}{\sqrt{R^2 + (X_C - X_L)^2}}$$


$$X_C = \frac{1}{\omega C} \quad ; \quad X_L = \omega L$$

Z is minimum when $\frac{1}{\omega C} = \omega L$


$$\Rightarrow \omega = \omega_0 = \sqrt{\frac{1}{LC}} \quad \text{Resonant frequency}$$

At resonance
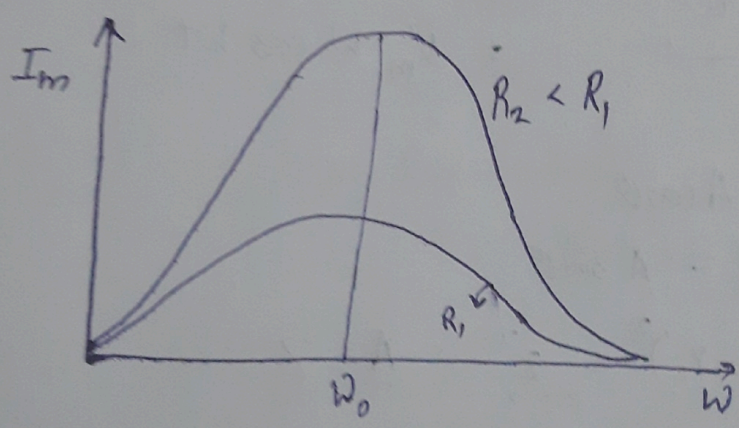
$$I_m = \frac{V_m}{R} \quad ; \quad \text{phase } \phi = 0$$




Both L & C must be present

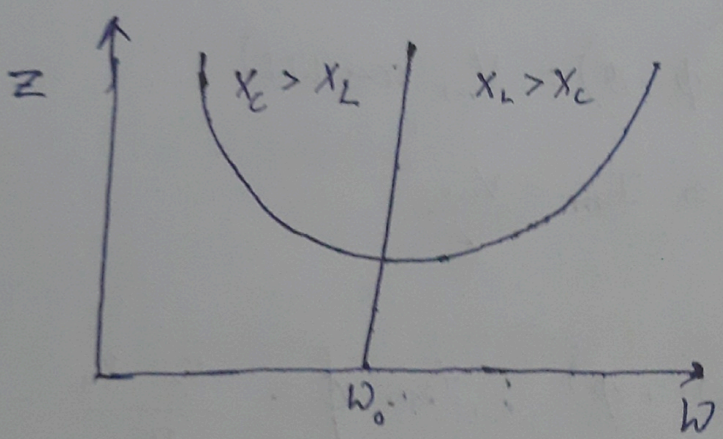

$$\text{If } \omega^2 > \omega_0^2 \\ \omega^2 > \frac{1}{LC}$$

$$I \propto \frac{1}{Z}$$

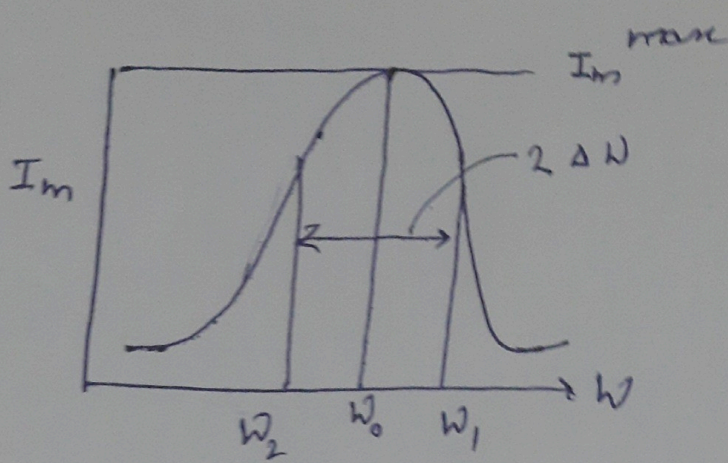$I^2 Z$ is maximum at $\omega = \omega_0$



Increase or decrease frequency (starting with ω_0) till power absorbed is half the maximum (at ω_0)

$$2\Delta\omega = (\omega_1 - \omega_2)$$

Band width (BW)

$$P = 0.5 I^2 R \rightarrow \text{at half power pt.}$$

$$= \left(\frac{I}{\sqrt{2}}\right)^2 R$$

Let

$$\omega_1 = \omega_0 + \Delta\omega$$

$$\omega_2 = \omega_0 - \Delta\omega$$

$$2\Delta\omega = \text{Bandwidth}$$

sharper resonance

→ Lower bandwidth

$$\text{At } \omega = \omega_1 \Rightarrow I_m = \frac{V_m}{\sqrt{R^2 + \left(\omega_1 L - \frac{1}{\omega_1 C}\right)^2}} \cong \frac{I_m^{\max}}{\sqrt{2}}$$

$$= \frac{V_m}{R \cdot \sqrt{2}}$$

By solving

$$\Delta\omega = \frac{R}{2L}$$

sharpness: $Q \rightarrow$ quality factor

$$\frac{\omega_0}{2\Delta\omega} = \frac{\omega_0 L}{R} \equiv Q$$