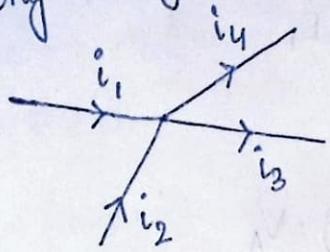


NCERT EXAMPLE PROBLEMS:

7. Kirchoff junction rule is a reflection of [More than one answer correct]
- a) Conservation of current density vector
 - b) Conservation of charge
 - c) the fact that the momentum with which a charged particle approaches a junction is unchanged (as a vector) as the charged particle leaves the junction.
 - d) the fact that there is no accumulation of charges at a junction.

Answer: b, d.

• Junction rule \rightarrow At any junction, the sum of currents entering the junction is equal to the sum of currents leaving the junction.



$$i_1 + i_2 = i_3 + i_4$$

Algebraic sum of currents flowing towards any junction in an electric circuit is zero; i.e., charges are conserved in an electric network. \therefore (b) is correct.

• No charge gets accumulated at the junctions as the total current flowing in must be equal to the total current flowing out. \therefore (d) is correct.