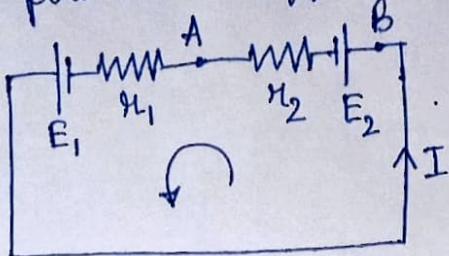


24. The circuit figure shows 2 cells connected in opposition to each other. Cell E_1 is of e.m.f 6V and internal resistance 2Ω , cell E_2 is of e.m.f 4V and internal resistance 8Ω . Find the potential difference between points A & B.



$$\begin{array}{l|l} E_1 = 6V & E_2 = 4V \\ r_1 = 2\Omega & r_2 = 8\Omega \end{array}$$

Answer:

$$-4 - 8I - 2I + 6 = 0$$

Cell E_2 e.m.f Internal resistance of E_2 Internal resistance of E_1 Cell E_1 e.m.f

$$\Rightarrow I = 0.2 \text{ A}$$

$$\text{Now, } V_B - 4 - (0.2 \times 8) = V_A$$

$$\therefore \boxed{V_B - V_A = 5.6 \text{ V}}$$

Note: sign convention for Kirchoff's law,

- (i) change of potential in traversing a resistance in the direction of current is $(-IR)$ while in the opposite direction is $(+IR)$
- (ii) change of potential in traversing an e.m.f source from negative to positive terminal is $+E$ while in the opposite direction $-E$ irrespective of direction of current.