

energy?

**7.15** Draw the effective equivalent circuit of the circuit shown in Fig 7.1, at very high frequencies and find the effective impedance.

**7.16** Study the circuits (a) and (b) shown in Fig 7.2 and answer the following questions.

$R$

$R$   $C$   $L$

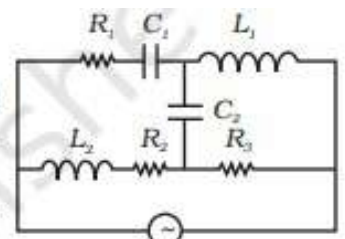


Fig. 7.1


$$15. \quad X_C = \frac{1}{\omega C} = \frac{1}{(2\pi\nu)C} \Rightarrow X_C \propto \frac{1}{\nu}$$

$$X_L = \omega L = (2\pi\nu)L \Rightarrow X_L \propto \nu$$

As frequency is very high;  $\nu \uparrow$

So,  $X_C \approx 0$  and  $X_L$  becomes too high  
 (Short circuited) (Open circuit)

Hence, equivalent circuit is:-

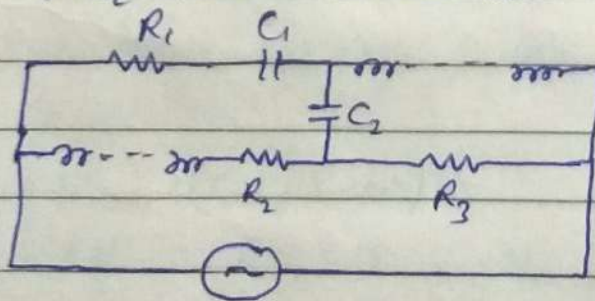

$$(X_{C1} = X_{C2} \approx 0)$$

Hence, total impedance  $\Rightarrow Z = R_1 + R_3$