

- 7.6** An inductor of reactance  $1 \Omega$  and a resistor of  $2 \Omega$  are connected in series to the terminals of a  $6 \text{ V}$  (rms) a.c. source. The power dissipated in the circuit is
- (a)  $8 \text{ W}$ .
  - (b)  $12 \text{ W}$ .
  - (c)  $14.4 \text{ W}$ .
  - (d)  $18 \text{ W}$ .

6. We know that average power dissipated in an L-R circuit is:-

$$P_{av} = (E_{rms})(I_{rms}) \cos \phi$$

$$X_L = 1 \Omega, \quad R = 2 \Omega, \quad V_{rms} = 6V \quad (\text{Given})$$

$(X_R)$

$$\begin{aligned} \therefore Z &= \sqrt{X_R^2 + X_L^2} \\ &= \sqrt{4 + 1} \\ &= \sqrt{5} \Omega \end{aligned}$$

$$\text{Hence, } P_{av} = (E_{rms}) \left( \frac{E_{rms}}{Z} \right) \left( \frac{R}{Z} \right) \quad \left( \because \cos \phi = \frac{R}{Z} \right)$$

$$\Rightarrow P_{av} = \frac{(\epsilon_{rms})^2 R}{(Z)^2}$$

$$= \frac{(6)^2 (2)}{(5)^2} = \frac{72}{5} = 14.4 \text{ W}$$

$$\therefore \boxed{P_{av} = 14.4 \text{ W}}$$

$\Rightarrow$  option (c) is the answer.