

- 7.18** In series LCR circuit, the plot of  $I_{\max}$  vs  $\omega$  is shown in Fig 7.3. Find the bandwidth and mark in the figure.


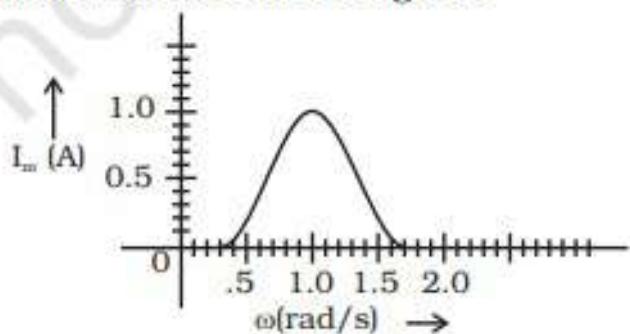


Fig. 7.3

1d. Band width  $\Rightarrow (\omega_2 - \omega_1)$

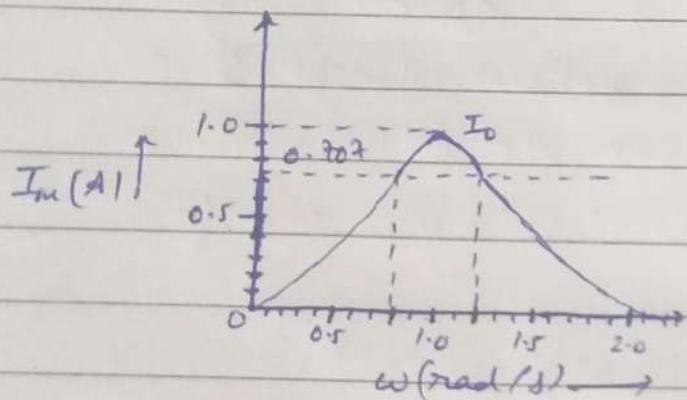where  $\omega_1$  and  $\omega_2$  are two frequencies where current becomes  $\frac{1}{\sqrt{2}}$  times the current value at resonant frequency.



$$\frac{I_m}{I_{max}} = \frac{I_0}{\sqrt{2}} = 1 A$$

From graph,

$$\omega_1 = 0.8 \text{ rad/s} \text{ and } \omega_2 = 1.2 \text{ rad/s}$$
$$\Rightarrow \text{Band width} = 1.2 - 0.8$$

$$= 0.4 \text{ rad/s}$$