

- 7.27** An electrical device draws 2kW power from AC mains (voltage 223V (rms) = $\sqrt{50,000}$ V). The current differs (lags) in phase by ϕ ($\tan \phi = \frac{-3}{4}$) as compared to voltage. Find (i) R , (ii) $X_C - X_L$, and (iii) I_M . Another device has twice the values for R , X_C and X_L . How are the answers affected?

27. $P = 2000 \text{ W}$; As current lags voltage ; so
 $V^2 = 50,000$; $\tan \phi = -\frac{3}{4}$

$$\text{As } P = \frac{V^2}{Z}$$

$$\Rightarrow 2000 = \frac{50000}{Z}$$

$$\Rightarrow \boxed{Z = 25 \Omega}$$

$$\Rightarrow Z = \sqrt{R^2 + (X_C - X_L)^2}$$

$$\Rightarrow (25)^2 = R^2 + (X_C - X_L)^2 \quad \text{--- (1)}$$

$$\Rightarrow \tan \phi = \frac{-3}{4}$$

$$\Rightarrow \frac{X_C - X_L}{R} = \frac{-3}{4} \quad \text{--- (2)}$$

$$\Rightarrow (X_C - X_L)^2 = \frac{9R^2}{16} \quad \text{--- (3)}$$

From (1) & (3)

$$R^2 = 16 \times 25$$

$$\Rightarrow \boxed{R = 20 \Omega}$$

From (2)

$$X_C - X_L = \left(\frac{-3}{4}\right) (20)$$

$$\Rightarrow \boxed{X_C - X_L = -15 \Omega}$$

$$I_{rms} = \frac{V}{Z} = \frac{223}{25} \approx 9 \text{ A}$$

$$\begin{aligned} \therefore I_0 &= \sqrt{2} I_{rms} \\ &= 9\sqrt{2} \text{ A} \\ &= 12.6 \text{ A} \end{aligned}$$

When all R , X_C , X_L are doubled; then

$$\tan \phi = \frac{X_C - X_L}{R} \text{ will remain same.}$$

When Z is doubled; $I = \frac{V}{Z}$ becomes half as value of V doesn't change.

As I becomes half $P = VI$ will become again half as voltage remains same.