

- 7.4** To reduce the resonant frequency in an LCR series circuit with a generator
- (a) the generator frequency should be reduced.
 - (b) another capacitor should be added in parallel to the first.
 - (c) the iron core of the inductor should be removed.
 - (d) dielectric in the capacitor should be removed.

4. In a L-C-R circuit,

Resonant frequency $\Rightarrow \boxed{\omega_0 = \frac{1}{\sqrt{LC}}}$ rad/s

As $\omega_0 \propto \frac{1}{\sqrt{L}}$ & $\omega_0 \propto \frac{1}{\sqrt{C}}$

\Rightarrow To reduce ω_0 ; L or C has to be increased

Option (a) As ω_0 ~~doesn't~~ only depends on L & C; so, it
(X) cannot be decreased with generator frequency.

Option (b) Connecting two capacitors in parallel increases the
(✓) effective capacitance $\Rightarrow C_{\text{eff}}$ increases.

Option (c) Removing the iron core of the inductor decreases
(X) L_{eff} .

Option (d) As ~~C_{eff}~~ $C_{\text{eff}} \propto K$ (dielectric constant) \Rightarrow
(X) By removing the dielectric, C_{eff} decreases.

\Rightarrow Option (b) is the answer.