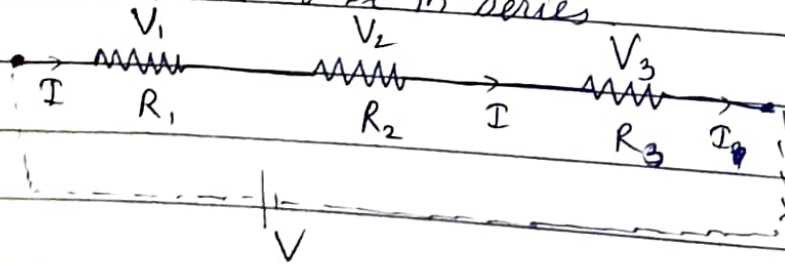


## Lecture 6 - Series and parallel Combination

### \* Series

Two resistors are said to be in series if only one of their end points is joined. If a 3<sup>rd</sup> resistor is joined together with the series combination of 2, then all 3 are said to be in series.



$$V = V_1 + V_2 + V_3$$

$$I R_{eq} = I R_1 + I R_2 + I R_3$$


$$I R_{eq} = I (R_1 + R_2 + R_3)$$

$$R_{eq} = R_1 + R_2 + R_3$$

∴ Equivalent Resistance of  $n$  resistors in series

$$R_{eq} = R_1 + R_2 + \dots + R_n$$

★ Parallel

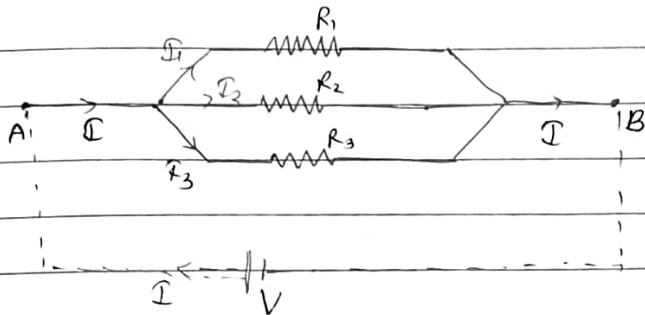

$$I = I_1 + I_2 + I_3$$

$$I = \frac{V}{R}$$

$$I = \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3}$$

$$\frac{V}{R_{eq}} = V \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)$$

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

∴ Equivalent Resistance of  $n$  resistors in parallel

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots + \frac{1}{R_n}$$

Two or more resistors are said to be in parallel if one end of all the resistors is joined together and similarly the other ends joined together.