

In a series resonant  $LCR$  circuit, the voltage across  $R$  is 100 volts and  $R = 1\text{ k}\Omega$  with  $C = 2\mu\text{F}$ . The resonant frequency  $\omega$  is  $200\text{ rad/s}$ . At resonance the voltage across  $L$  is

- A  $2.5 \times 10^{-2}\text{ V}$
- B  $40\text{ V}$
- C  $250\text{ V}$
- D  $4 \times 10^{-3}\text{ V}$

5. In given series LCR circuit,

$$V_{(\text{across } R)} = 100\text{V}, \quad R = 1\text{K}\Omega, \quad C = 2\mu\text{F}$$

~~100~~ = 1000  $\Omega$  =  $2 \times 10^{-6}\text{F}$

$$\text{Resonant frequency } (\omega_0) = 200 \text{ rad/s}$$

$$\text{Also, } \omega_0 = \frac{1}{\sqrt{LC}}$$

$$\Rightarrow 200 = \frac{1}{\sqrt{L \times 2 \times 10^{-6}}}$$

$$\Rightarrow L = \frac{100}{8} \text{ H}$$

$$\text{Now, } V_{(\text{across } R)} = I \cdot R$$

$$\Rightarrow 100 = (I) 1000$$

$$\Rightarrow \boxed{I = 0.1 \text{ A}}$$

$$V_{(\text{across } L)} = I(X_L)$$

$$= (0.1)(\omega L)$$

$$= (0.1)(200) \left( \frac{100}{8} \right)$$

$$\boxed{V_{(\text{across } L)} = 250\text{V}}$$