

In a series  $LCR$  circuit  $R = 200\Omega$  and the voltage and the frequency of the main supply is  $220V$  and  $50\text{ Hz}$  respectively. On taking out the capacitance from the circuit the current lags behind the voltage by  $30^\circ$ . On taking out the inductor from the circuit the current leads the voltage by  $30^\circ$ . The power dissipated in the  $LCR$  circuit is

- A  $305\text{ W}$
- B  $210\text{ W}$
- C  $zero\text{ W}$
- D  $242\text{ W}$

4. In given LCR circuit,

$$R = 200 \Omega \text{ and } V_{\text{rms}} = 220 \text{ V}, \nu = 50 \text{ Hz}$$

$$\Rightarrow \omega = 2\pi\nu \Rightarrow \frac{100\pi \text{ rad/s}}$$

When capacitor is taken out, then it becomes L-R:-

$$\Rightarrow \tan \phi = \frac{X_L}{R} \quad (\phi = 30^\circ \text{ given})$$

$$\Rightarrow \tan 30^\circ = \frac{X_L}{200}$$

$$\Rightarrow X_L = \frac{200 \Omega}{\sqrt{3}}$$

When inductor is taken out, then it becomes R-C circuit:-

$$\therefore \tan \phi = \frac{X_C}{R} \quad (\phi = 30^\circ \text{ given})$$

$$\Rightarrow \tan 30^\circ = \frac{X_C}{200}$$

$$\Rightarrow X_C = \frac{200 \Omega}{\sqrt{3}}$$

$$\text{Now, } X_C - X_L = \frac{200}{\sqrt{3}} - \frac{200}{\sqrt{3}} \Rightarrow 0$$

$$\therefore Z = \sqrt{R^2 + (X_C - X_L)^2}$$
$$= \sqrt{(200)^2 + 0}$$

$$\Rightarrow \boxed{Z = 200 \Omega}$$

$$\begin{aligned} \text{Hence } P_{\text{dissipated}} &= (E_{\text{rms}})(I_{\text{rms}}) \cos \phi \\ &= (E_{\text{rms}}) \left( \frac{E_{\text{rms}}}{Z} \right) \left( \frac{R}{Z} \right) \quad \left( \because \cos \phi = \frac{R}{Z} \right) \\ &= \frac{(E_{\text{rms}})^2 R}{(Z)^2} \\ &= \frac{(220)^2 (200)}{(200)^2} \end{aligned}$$

$$P_{\text{dissipated}} = 242 \text{ W}$$