

**7.5** Which of the following combinations should be selected for better tuning of an  $LCR$  circuit used for communication?

- (a)  $R = 20 \Omega$ ,  $L = 1.5 \text{ H}$ ,  $C = 35\mu\text{F}$ .
- (b)  $R = 25 \Omega$ ,  $L = 2.5 \text{ H}$ ,  $C = 45\mu\text{F}$ .
- (c)  $R = 15 \Omega$ ,  $L = 3.5 \text{ H}$ ,  $C = 30\mu\text{F}$ .
- (d)  $R = 25 \Omega$ ,  $L = 1.5 \text{ H}$ ,  $C = 45\mu\text{F}$ .

5. For better tuning of LCR circuit, Quality factor must be high.

$$Q = \frac{1}{R} \sqrt{\frac{L}{C}}$$

On checking the above options by putting given values;  
Option (c) (i.e.  $R = 15 \Omega$ ,  $L = 3.5 \text{ H}$ ,  $C = 30 \mu\text{F}$ ) given the maximum value of  $Q$ .

$\Rightarrow$  Option (c) is the answer.