


7.24 A 60 W load is connected to the secondary of a transformer whose primary draws line voltage. If a current of 0.54 A flows in the



Alternating Current

load, what is the current in the primary coil? Comment on the type of transformer being used.

24. $P_s = 60\text{W}$, $I_s = 0.54\text{A}$ (given) & $V_p = 220\text{V}$

$$\therefore P_s = V_s I_s$$

$$\Rightarrow 60 = V_s (0.54)$$

$$\Rightarrow \boxed{V_s = \frac{1000}{9}\text{V}}$$

(Here; subscript P is for primary coil and
subscript S is for secondary coil.)

$$\text{Now, } \frac{V_s}{V_p} = \frac{1000/9}{220} \approx \frac{1}{2} < 1$$

(As $\frac{V_s}{V_p} < 1 \Rightarrow$ Transformer is step-down)

In a transformer, Output power = Input power

$$\Rightarrow I_s V_s = I_p V_p$$

$$\Rightarrow (0.54) \left(\frac{1000}{9} \right) = I_p (220)$$

$$\Rightarrow I_p = \frac{6}{22}$$

22

$$\Rightarrow \boxed{I_p = 0.272\text{A}}$$