

Resistance




Current I is same

$$V = V_1 + V_2 + \dots + V_n$$

$$I_{\text{Req}} = IR_1 + IR_2 + \dots + IR_n$$
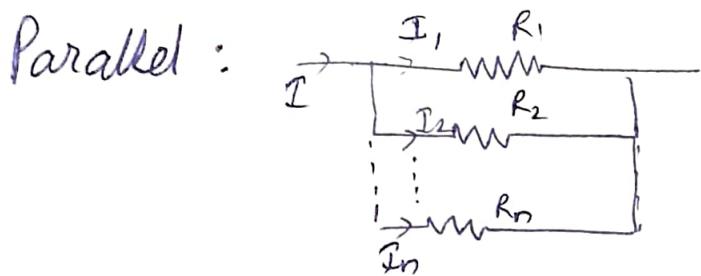
$$\therefore R_{\text{Req}} = R_1 + R_2 + \dots + R_n$$



V is same

$$I = I_1 + I_2 + \dots + I_n$$

$$\frac{V}{R_{\text{Req}}} = \frac{V}{R_1} + \frac{V}{R_2} + \dots + \frac{V}{R_n}$$

$$\frac{1}{R_{\text{Req}}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}$$