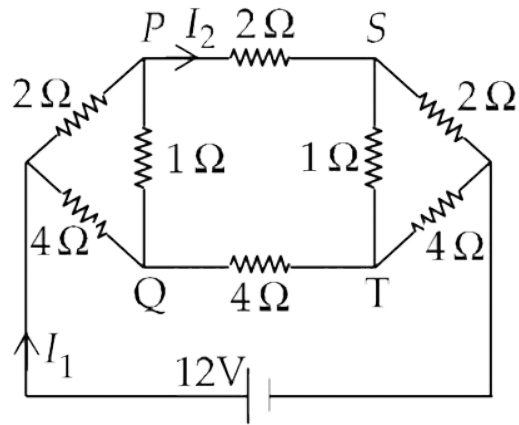


Problem) For the resistance network shown in the figure, choose the correct option(s).
 [JEE 2012; Paper-1, 4/66]



- (A) The current through PQ is zero. (B) $I_1 = 3 \text{ A}$.
 (C) The potential at S is less than that at Q. (D) $I_2 = 2 \text{ A}$.

Answer:- A,B,C,D