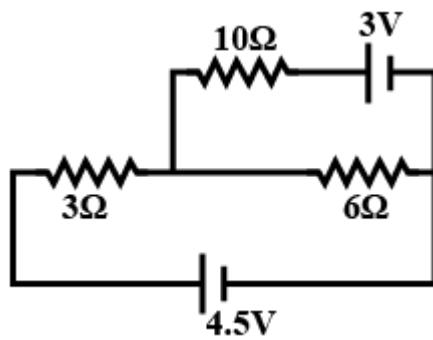


Problem) Find the current through the $10\ \Omega$ resistor shown in figure



- 1) zero
- 2) 1A
- 3) 2A
- 4) 5A