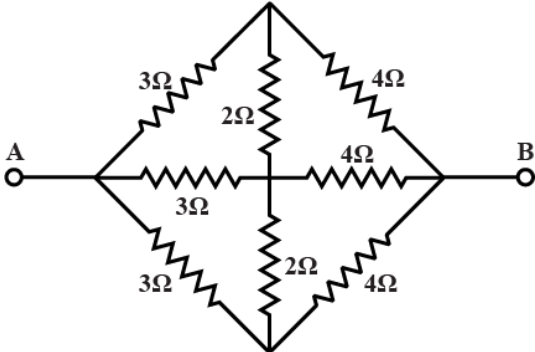


Problem) The equivalent resistance between A and B will be:



- (A) $2/7$
- (B) 8
- (C) $4/3$
- (D) $7/3$