

20 V 10 V 2 V 1 V

10. A moving coil galvanometer, having a resistance G , produces full scale deflection when a current I_g flows through it. This galvanometer can be converted into (i) an ammeter of range 0 to I_0 ($I_0 > I_g$) by connecting a shunt resistance R_A to it and (ii) into a voltmeter of range 0 to V ($V = GI_0$) by connecting a series resistance R_V to it. Then,

[12 April 2019, III]

$$(a) \quad R_A R_V = G^2 \left(\frac{I_0 - I_g}{I_g} \right) \text{ and } \frac{R_A}{R_V} = \left(\frac{I_g}{I_0 - I_g} \right)^2$$

$$(b) \quad R_A R_V = G^2 \text{ and } \frac{R_A}{R_V} = \left(\frac{I_g}{I_0 - I_g} \right)^2$$

$$(c) \quad R_A R_V = G^2 \left(\frac{I_g}{I_0 - I_g} \right) \text{ and } \frac{R_A}{R_V} = \left(\frac{I_0 - I_g}{I_g} \right)^2$$

$$(d) \quad R_A R_V = G^2 \text{ and } \frac{R_A}{R_V} = \frac{I_g}{(I_0 - I_g)}$$

(b) In an ammeter,

$$i_g = i_0 \frac{R_A}{R_A + G}$$

and for voltmeter,

$$V = i_g (G + R_V) = G i_0$$

On solving above equations, we get

$$R_A R_V = G^2$$

$$\text{and } \frac{R_A}{R_V} = \left(\frac{i_g}{i_0 - i_g} \right)^2$$