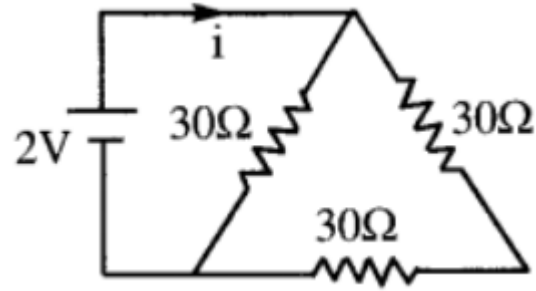


Example 4) The current i in the circuit (see fig) is



- a) $(1/45)$ ampere
- b) $(1/15)$ ampere
- c) $(1/10)$ ampere
- d) $(1/5)$ ampere

Solution-

(c) BC and CA are in series.


$$\therefore R_{BCA} = 30 + 30 = 60\Omega$$

BCA and BA are in parallel,

$$\therefore \frac{1}{R_{eq}} = \frac{1}{60} + \frac{1}{30} = \frac{3}{60} = \frac{1}{20}$$

$$\therefore R_{eq} = 20\Omega$$
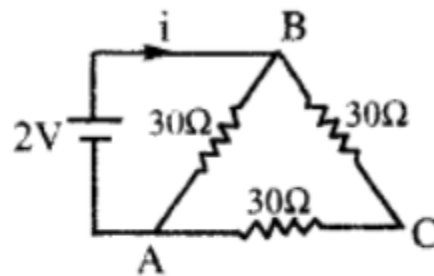
$$\text{or } i = \frac{2\text{volt}}{20\Omega} = 0.1\text{A}$$



$$\therefore i = \frac{V}{R_{eq}}$$