

7.23 A coil of 0.01-henry inductance and 1-ohm resistance is connected to 200 volt, 50 Hz ac supply. Find the impedance of the circuit and time lag between max. alternating voltage and current.

Answer:

Inductance  $L = 0.01 \text{ H}$

Resistance  $R = 1 \text{ ohm}$

Voltage = 200 V

Frequency = 50 Hz

Impedance =  $Z = 3.3 \text{ ohms}$

Phase difference =  $72 \times \pi/180 \text{ rad}$

Time lag in the alternating voltage and the current is 0.004 sec