

7.27 An electrical device draws 2kW power from AC mains (voltage 223V (rms) = 50,000 V). The current differs (lags) in phase by  $\varphi$  ( $\tan \varphi = -3/4$ ) as compared to voltage. Find (i) R, (ii)  $X_C - X_L$ , and (iii)  $I_m$ . Another device has twice the values for R,  $X_C$  and  $X_L$ . How are the answers affected?

Answer:

Impedance =  $Z = 25$  ohms

$$635 = 25R^2/16$$

a) Resistance =  $R = \sqrt{25 \times 16} = \sqrt{400} = 20$  ohms

b)  $X_C - X_L = -3R/4 = -15$  ohms

c) Main current =  $I_m = 12.6$  A