

**Q10: An arc lamp requires a direct current of 10A at 80V to function. If it is connected to a 220V (RMS), 50 Hz AC supply, the series inductor needed for it to work is close to**

- (a) 0.065 H
- (b) 80 H
- (c) 0.08 H
- (d) 0.044 H

**Solution**

$$I = 10\text{A}$$

$$V = 80\text{ V}$$

$$R = 8\ \Omega$$

$$10 = 220 / (8^2 + X_L^2)^{1/2}$$

$$64 + X_L^2 = 484$$

$$X_L = \sqrt{420}$$

$$2\pi \times 50L = \sqrt{420}$$

$$L = \sqrt{420} / 100\pi$$

$$L = 0.065\text{ H}$$

**Answer: (a) 0.065 H**