

In a series RLC , circuit $R = 30 \Omega$, $L = 15 \text{ mH}$, and $C = 51 \mu\text{F}$. If the source voltage and frequency are 12 V and 60 Hz , respectively, what is the current in the circuit?

$$X_L = 2 * 3.14 * 60 * 0.015 = 5.655\Omega$$

$$X_C = \frac{1}{2 * 3.14 * 60 * 0.000051} = 5.655\Omega$$

$$Z = \sqrt{30^2 + (52 - 5.655)^2} = 55.21\Omega$$

$$I = \frac{12}{55.21} = 217\text{mA}$$