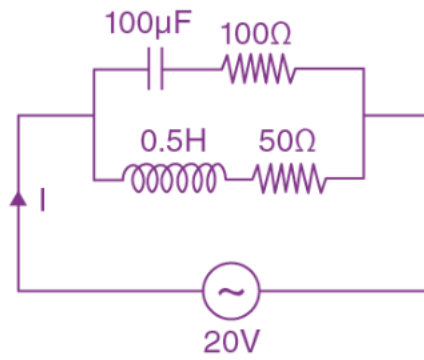


Question 6) In the given circuit, the AC source has $\omega = 100 \text{ rad/s}$. Considering the inductor and capacitor to be ideal, the correct choice (s) is(are)



- (A) The current through the circuit, I is 0.3 A .
- (B) The current through the circuit, is $0.3\sqrt{2} \text{ A}$.
- (C) The voltage across 100Ω resistor is $10\sqrt{2} \text{ V}$.
- (D) The voltage across 50Ω resistor is 10 V .

Solution:

In the upper branch the net impedance, ($C = 100\mu\text{F}$, $R = 100\Omega$)

Therefore, the net impedance will be

$$Z_1 = \sqrt{\frac{1}{(\omega C)^2} + R^2}$$

$$Z_1 = \sqrt{\frac{1}{(100 \times 100 \times 10^{-6})^2} + 100^2}$$

$$= 100\sqrt{2}$$

$$\text{Current } I_1 = V/Z_1 = 20/(100\sqrt{2})$$

$$\cos \Phi_1 = R/(100\sqrt{2})$$

$$= 100/(100\sqrt{2})$$

$$= 1/\sqrt{2}$$

$$\Rightarrow \Phi_1 = 45^\circ$$

In the lower branch the net impedance ($L = 0.5 \text{ H}$, $R = 50 \Omega$)

Therefore, the net impedance will be

$$Z_2 = \sqrt{(\omega L)^2 + R^2}$$

$$Z_2 = \sqrt{(0.5 \times 100)^2 + 100^2}$$

$$= 50\sqrt{2}$$

$$\text{Current, } I_2 = V/Z_2$$

$$= 20/(50\sqrt{2})$$

$$\cos \Phi_1 = R/(50\sqrt{2})$$

$$= 50/(50\sqrt{2})$$

$$= 1/\sqrt{2}$$

$$\Rightarrow \Phi_1 = 45^\circ$$

Thus the total current I is given by the summation of I_1 and I_2 which differ by 90° in phase and hence

$$I = \sqrt{I_1^2 + I_2^2}$$

$$= (1/\sqrt{10}) \text{ A} \approx 0.3 \text{ A}$$

$$\text{Voltage across } 100 \Omega = I_1 R_1 = [20/(100\sqrt{2})] \times 100 = 10\sqrt{2} \text{ V}$$

$$\text{Voltage across } 50 \Omega = I_2 R_2 = [20/(50\sqrt{2})] \times 50 = 10\sqrt{2} \text{ V}$$