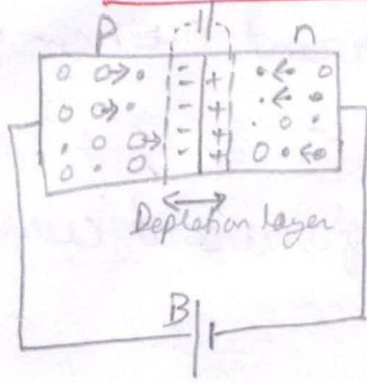


# Biasing of P-N Junction

## i) Forward biasing



Positive terminal of ext. battery (B) is connected to p-side & -ive to n side of P-n Junction.

- Applied voltage  $V$  of B mostly drops across depletion region as its resistance is very high ( $\because$  No free charge carrier).
- Forward voltage oppose potential barrier  $V_B$   $\therefore$  height of pot. barrier is reduced & width of depletion layer decreased.

$$\text{effective height} = V_B - V$$

- Forward current - due to migration of Majority carriers across P-n Junction.

## ii) Reverse biasing: -ive terminal of ext. Battery (B) is connected to p & +ive to n-side.

- applied voltage ( $V$ ), drop across depletion region & its direction of voltage is same as that of potential barrier.  $\therefore$  barrier height inc.

& width of depletion region inc.

$$\text{effective barrier height } (V_B + V)$$

Reverse current - As no motion of majority carriers So by minority charge carriers.

\* Resistance of p-n Junction is low to flow of current when forward biased.


\* High to flow of current when Reverse biased.

\* → Pot. barrier oppose the forward current & support reverse current.

## ⇒ Characteristic of P-N Junction Diode.
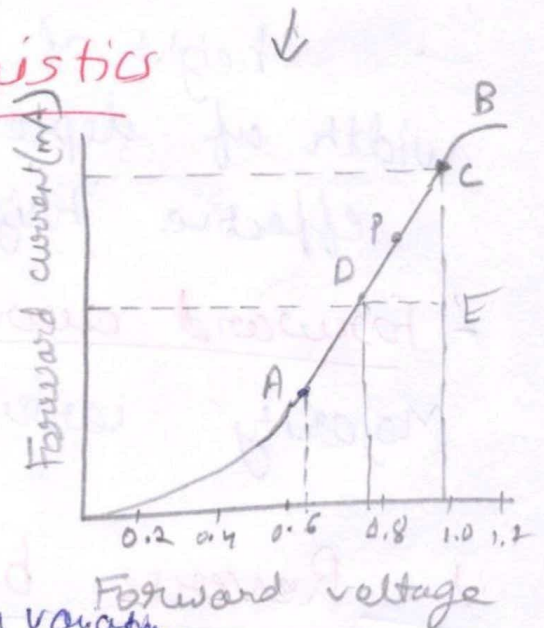
### (i) Forward characteristics

Knee voltage: it is forward voltage beyond which the current through junction starts increasing rapidly with voltage - linear variation.



But below knee voltage - Non-linear variation.

Dynamic Resistance


$$r_D = \frac{DE}{CE}$$

## (ii) Reverse characteristics

From graph:

Reverse current is very small & is voltage independent upto certain reverse bias voltage

known as Breakdown voltage

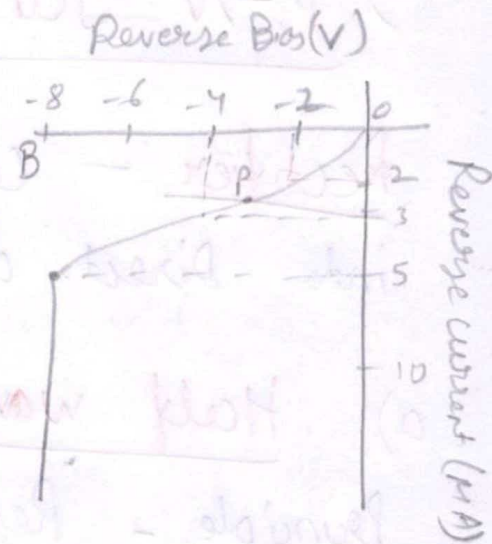

If reverse bias voltage is = OB (breakdown voltage) the reverse current will increase abruptly.

Dynamic Resistance — Ratio of small change in voltage  $\Delta V$  applied across P-n Junction to small change in junction current  $\Delta I$ .


$$R_d = \frac{\Delta V}{\Delta I} = \frac{DE}{CE}$$

# → P-N Junction Diode As a Rectifier

Rectifier - Convert Alt. current/voltage into Direct current/voltage.
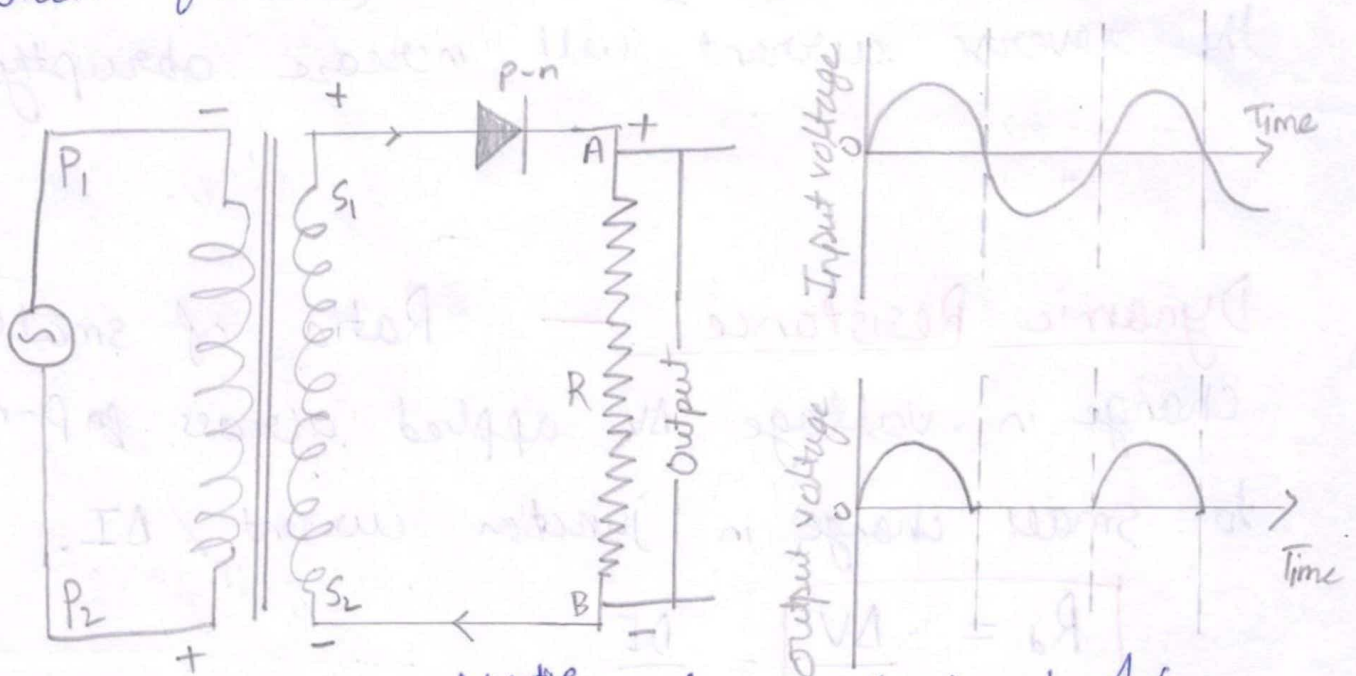
## a) Half wave Rectifier

Principle - Resistance of P-n Junction become low when forward biased & high when reverse biased.






• Working During ~~the~~ <sup>Negative</sup> half cycle of input A.C.

let  $P_1$  be +ive &  $P_2$  be -ive so due to induction  $S_1$  become -ive &  $S_2$  +ive. i.e. P-n Junction is reverse biased. So High resistance → No current → No output.

→ Working During +ive half cycle of input A.C.

$P_1$  be -ive &  $P_2$  +ive. so by induction  $S_1$  become +ive &  $S_2$  -ive. i.e. P-n Junction is forward biased so low resistance → current flows → output across ~~work~~ load.
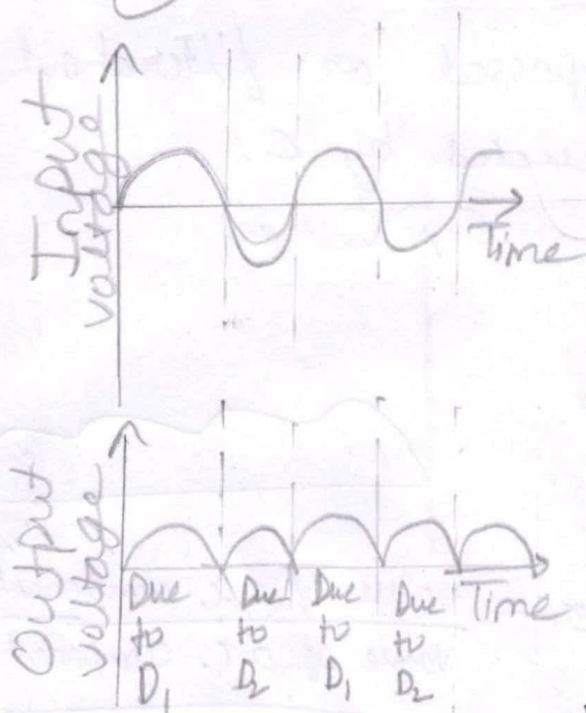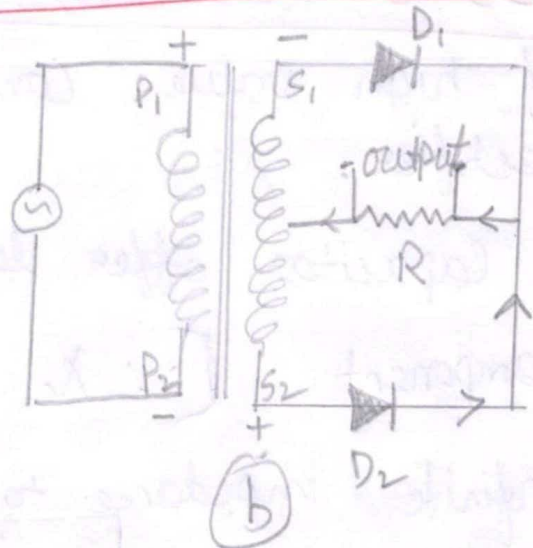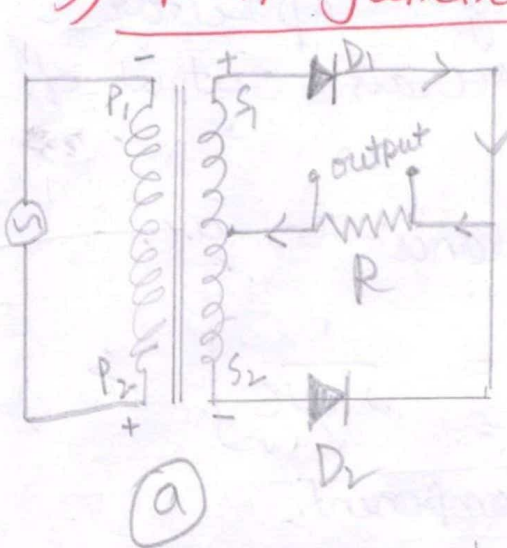
## b) P-n junction diode as Full wave rectifier



During positive half cycle of input A.C.,  $D_1$  is forward biased &  $D_2$  is reverse biased. So forward current flows on account of majority carriers of junction Diode  $D_1$ .

During Negative half cycle,  $D_2$  is forward &  $D_1$  is reverse biased.

So forward current flows due to  $D_2$ .

\* In both halves, current through  $R$  flows in same direction

However the output signal voltage is having ripple content. i.e., d.c. component & A.C. component.

It can be made d.c. by filtering with a Filter circuit.



Filter circuit — Single capacitor C of high value connected across output of rectifier.

Capacitor offer low impedance to a.c.

Component  $\left[ \because X_c = \frac{1}{\omega C} = \frac{1}{2\pi f C} \right] \nearrow$

infinite impedance to d.c. component.

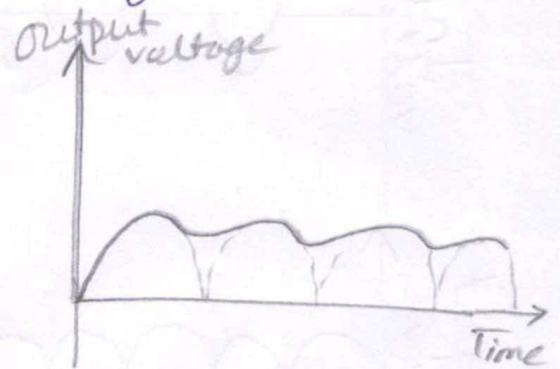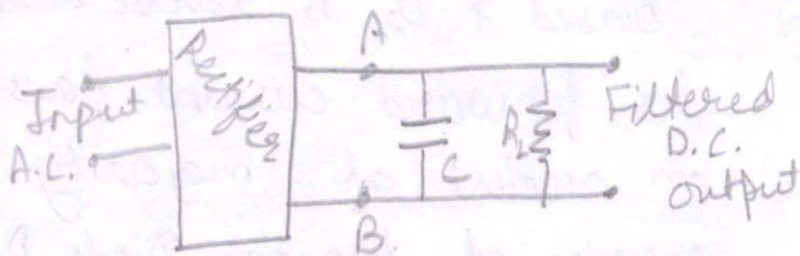$\therefore$  A.c. component is bypassed or filtered out  
D.C. component obstructed by C.



Ripple factor of rectifier =  $\frac{\text{value of a.c. component}}{\text{value of d.c. component}}$

$$= \frac{I_{a.c.}}{I_{d.c.}} = \frac{E_{a.c.}}{E_{d.c.}} = \sqrt{\left( \frac{I_{r.m.s.}}{I_{d.c.}} \right)^2 - 1}$$

Efficiency of rectifier,  $\eta = \frac{\text{output d.c. power} \times 100}{\text{input A.C. power}}$

$\eta$  for half wave rectifier = 40.6%  $\rightarrow$  so of very little use.

$\eta$  " full " " = 81.2%