
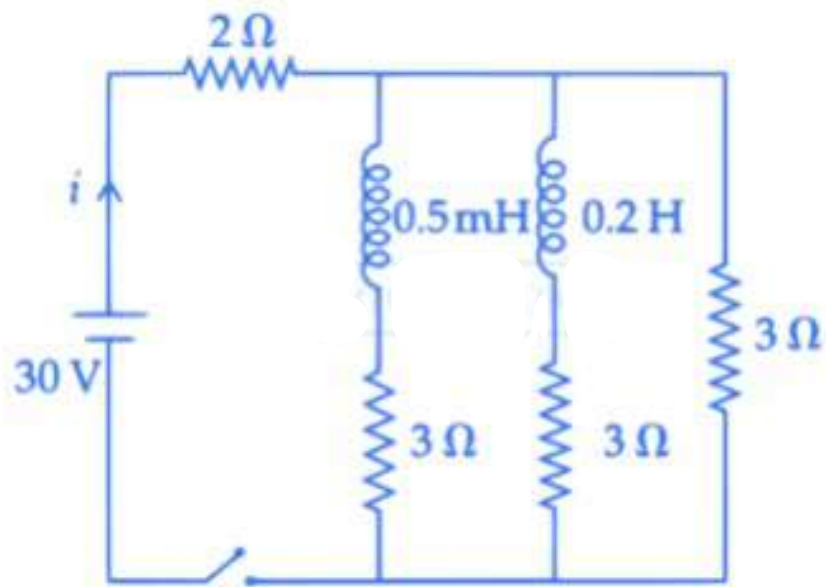


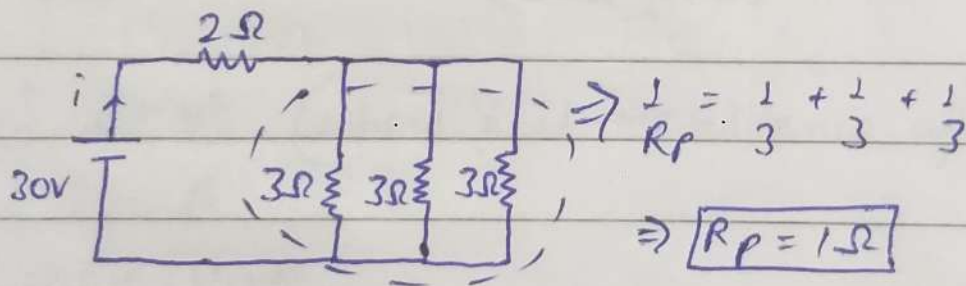For the given circuit the current  $i$  through the battery when the key is closed and the steady state has been reached is \_\_\_\_\_ (JEE MAIN 2021)




- A 6 A
- B 25 A
- C 10 A
- D 0 A

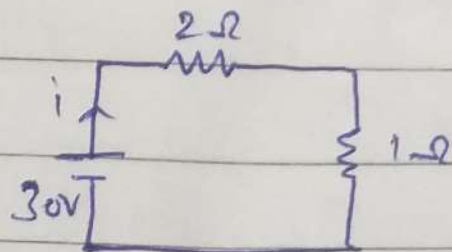2. When, key is closed, then, in steady state inductor becomes short circuited and offers no resistance. Hence, equivalent circuit becomes:-



$$\therefore R_{net} = 2 + 1 \Rightarrow 3\Omega$$



$$\therefore I = \frac{V}{R} = \frac{30}{3} \Rightarrow 10A$$

$$\Rightarrow \boxed{I = 10A}$$