
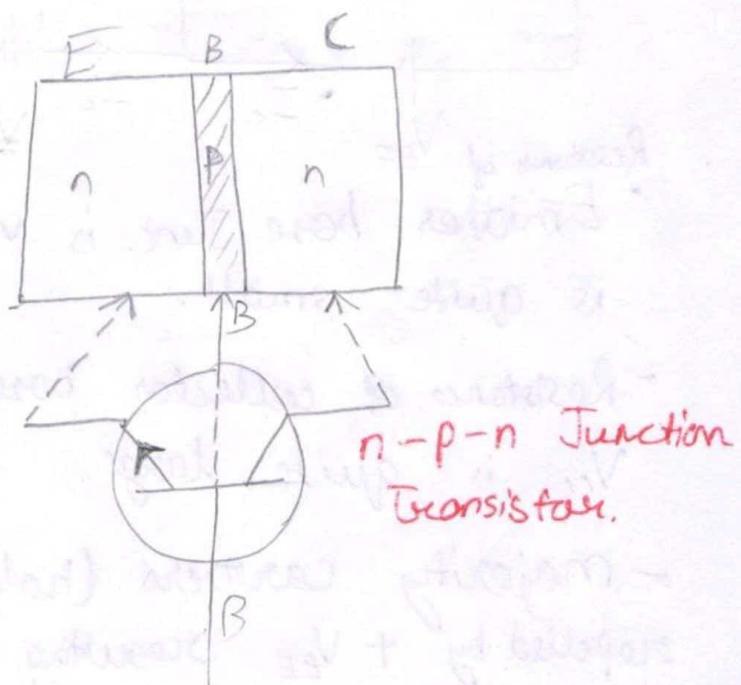


Junction Transistor

Obtained by growing a thin layer of one type semiconductor in b/w two thick layers of other similar type semiconductor.

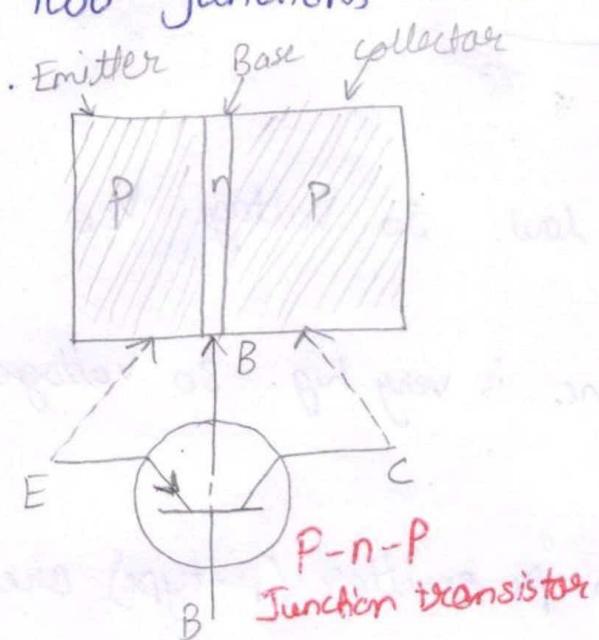→ Thus junction transistor is semiconductor device having two junctions & 3 terminals.



→ 3 layers of transistor

Emitter (E) - Left hand side thick layer, heavily doped

Base (B) - Central thin layer, lightly doped


Collector (C) - Right hand side thick layer, moderately doped.

→ functions: Emitter emits majority carriers.

Collector collect majority carriers.

Base provide proper interaction b/w emitter & collector

Working.

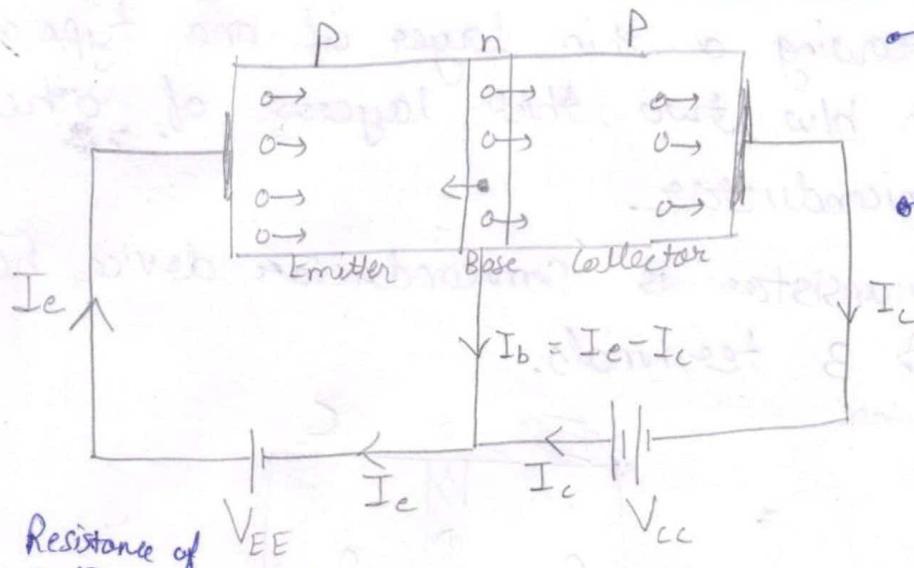

- Emitter base Junc. is forward biased.
- Collector base Junc. is reverse biased.

- Emitter base Junc. is very low. So voltage V_{EE} is quite small.
- Resistance of collector base Junc. is very high. So voltage V_{cc} is quite large.
- Majority carriers (holes) in P-emitter (P-type) are repelled by $+V_{EE}$ resulting in I_e .
- If base is lightly doped so only few holes get neutralised by e^- -hole combination, resulting in I_b .
- Remaining holes pass over to collector because of negative V_{cc} resulting in I_c .

[Motion of e^- from book]

→ Current in p-n-p transistor is carried by holes → at same time their conc. is maintained. But in external circuit current is due to flow of e^- . Direction shown by arrow. motion of e^- opp. to arrow.


$$I_e = I_b + I_c$$

* $I_e > I_c$ flow in opp. direction.

⇒ Modes of Study of Junction Transistor

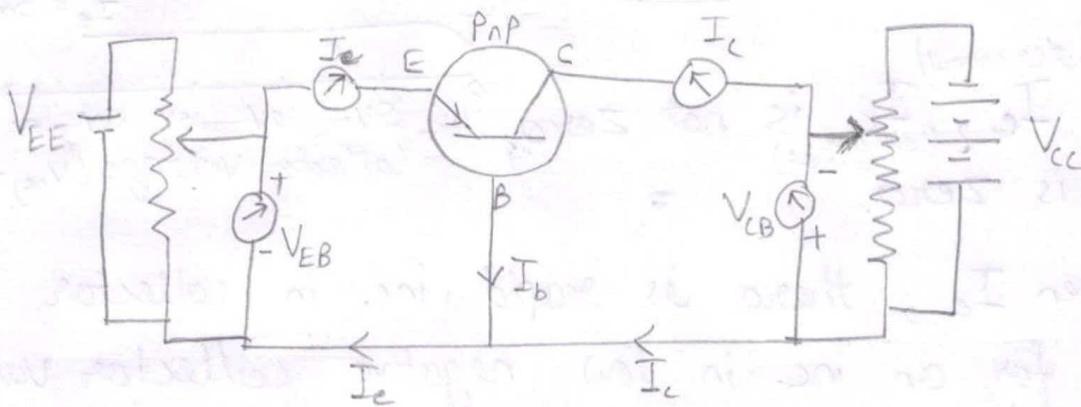- a) Common base config.
- b) Common emitter " & c) common collector config.

a). Common Base Transistor Characteristics




→ Emitter base circuit is forward biased with V_{EE}
Collector base " " " Reversed biased with V_{CC}

For current obey condition $I_e = I_b + I_c$

Input or Emitter characteristics

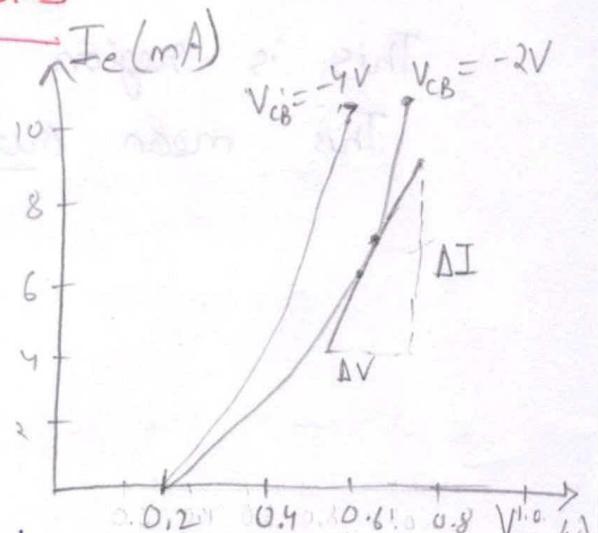Apply suitable constant voltage on collector & by applying various value of emitter voltage note corresponding value emitter current. Plot graph.




- i) for given collector voltage, I_e inc. rapidly with inc. value of emitter base voltage. i.e. input resistance is small.
- ii) for higher negative collector voltage, I_e rise more rapidly with collector voltage.
- Reciprocal to slope of line AB will give input resistance (R_i) of transistor.

$$\therefore R_i = \frac{\Delta V}{\Delta I} = \frac{AC}{BC}$$


Output or collector characteristics

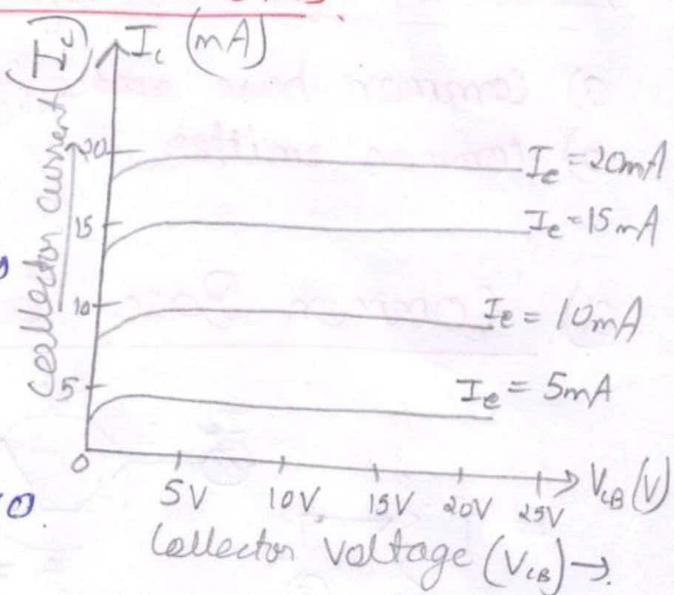Fix suitable constant value of emitter current & by applying various values of collector voltages note collector current. Graph→



- i) For given I_e , I_c is not zero when V_c is zero. (emitter current)
- ii) For given I_e , there is rapid inc. in collector current for an inc. in low negative collector voltage. This is region of low collector resistance. Transistor is never operated in this region.
- iii) For given I_e , I_c becomes saturated for a certain collector voltage shown by horizontal line. This is region of high collector resistance. This means output resistance is very high.

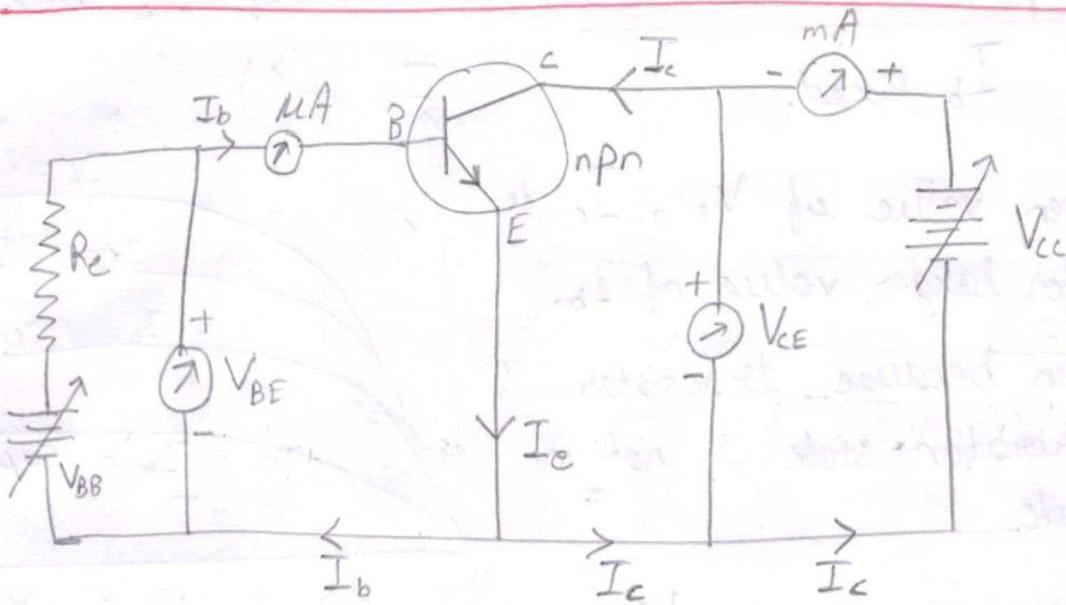b) Common Emitter Transistor characteristics



Input characteristics: Relation between $I_b \rightarrow V_{BE}$
Keeping V_{CE} Fixed.


- When V_{BE} is greater than barrier voltage, curve look similar to forward biased diode. More than 95% of emitter e⁻ go to collector to form I_c . That is why I_b is much smaller.

Input dynamic resistance of transistor (R_i) =

$$\frac{\text{Change in base-emitter voltage } (\Delta V_{BE})}{\text{Change in base current } (\Delta I_b)}$$

at constant $\Rightarrow V_{CE}$
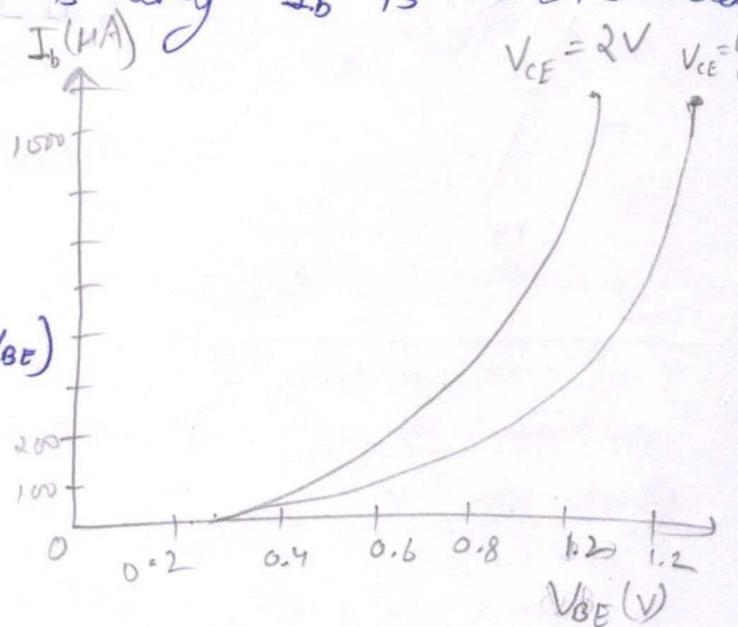
$$R_i = \left[\frac{\Delta V_{BE}}{\Delta I_b} \right]_{V_{CE} \text{ constant}}$$



The output characteristics Variation of I_c with V_{CE}

Keeping I_b fixed.

- For given value of V_{CE} , I_c is larger for larger value of I_b .

This happen because transistor is in saturation state & not in active state.

- As long as collector emitter junction is reverse biased ($V_{CE} > V_{BE}$) we get I_c which is independent of V_{CE} .
- Value of I_c is controlled by I_b .

Output dynamic resistance of transistor

$$R_o = \left[\frac{\Delta V_{CE}}{\Delta I_c} \right]_{I_b \text{ is constant}}$$

