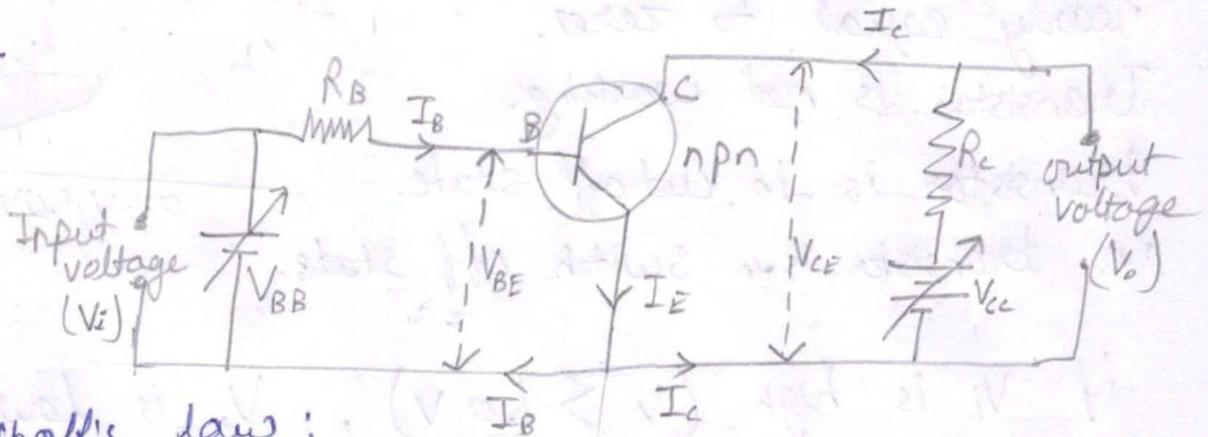


# Transistor As a Switch — for on/off of current in circuit

Here, we use npn transistor with common emitter transistor.



using Kirchhoff's law:

i) for input circuit:  $-V_{BB} + I_B R_B + V_{BE} = 0$

$\Rightarrow V_{BB} = I_B R_B + V_{BE}$  — (1)

for Si transistor  $V_{BE} = 0.6V$

ii) For output circuit:  $-V_{CC} + I_C R_C + V_{CE} = 0$

$\Rightarrow V_{CE} = V_{CC} - I_C R_C$  — (2)

let  $V_{BB}$  be d.c. input voltage ( $V_i$ ) &  $V_{CE}$  as output voltage ( $V_o$ )

$\therefore V_i = I_B R_B + V_{BE}$  &  $V_o = V_{CC} - I_C R_C$

→ Case 1: for Si transistor  $V_i < 0.6V$  :  $I_C = 0$ . Cut off state

Case 2 :  $V_i > 0.6V$  but less than  $1.0V$  : Some  $I_C$ .

if  $I_C$  increase,  $V_o$  decreases. but if  $V_i$  inc. beyond

$0.6V$ ,  $I_C$  increase almost linearly, so  $V_o$  decrease linearly till  $V_i$  becomes nearly  $1V$ . This is

active state of transistor.

Case 3 :  $V_i > 1.0V$  .

with inc in  $V_i$ ,  $V_o$  decrease towards zero but never becomes zero.


So, if  $V_i$  is (i.e.  $V_i < 0.6\text{ V}$ )

$V_o$  is high ( $= V_{cc}$ ) &  $I_c$  is nearly equal to zero.

Transistor is not working.

transistor is in cutoff state.

i.e. transistor is in switch off state.

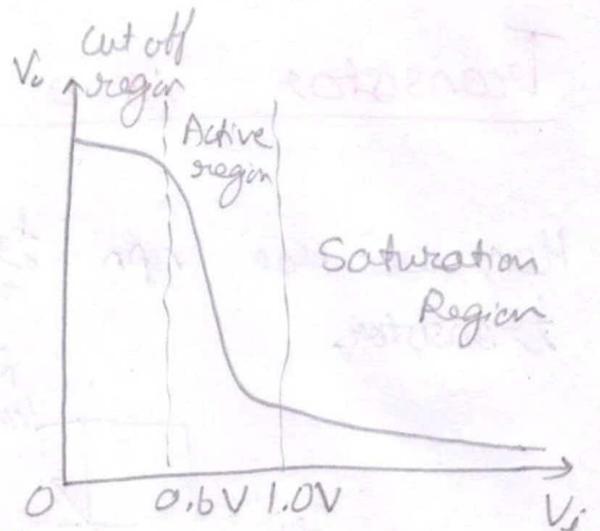


if  $V_i$  is high ( $V_i > 1.0\text{ V}$ ),  $V_o$  is low  $\approx 0$

$I_c$  is maximum or saturated.

Now transistor is fully conducting. i.e. Switch on state


→ Switching circuits are made in such a way that transistor does not remain in active states,

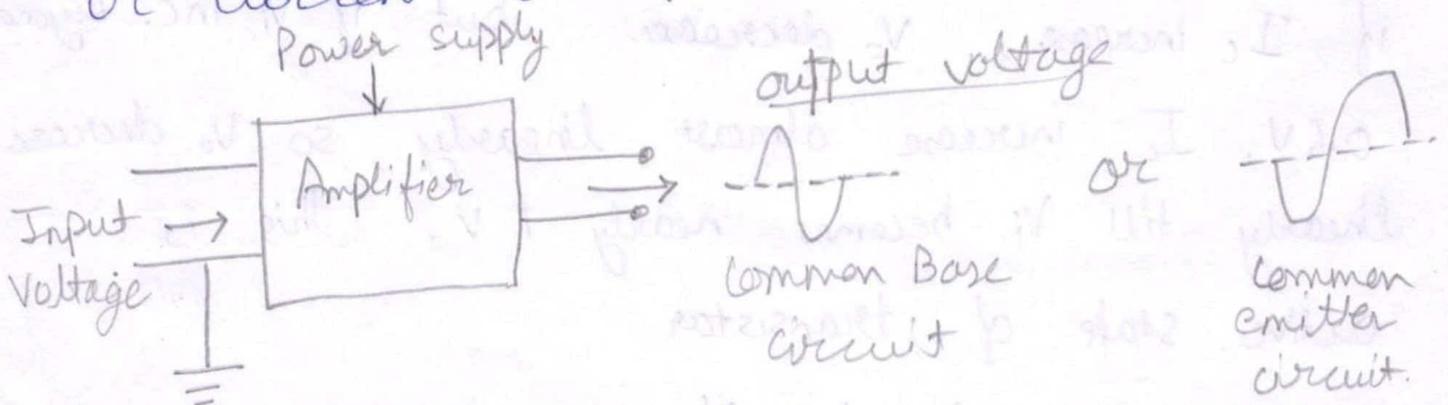Amplifier → used for increasing the amplitude of variation of alternating voltage or current or power.



# Transistor as Common Base Amplifier.

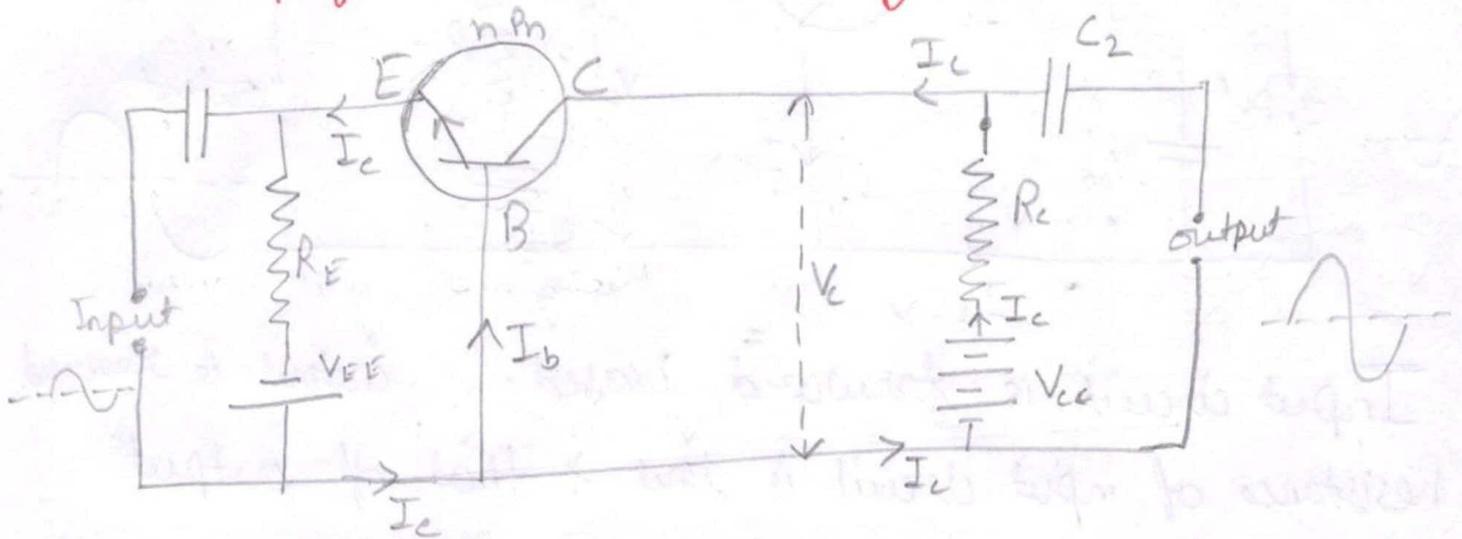a) Amplifier circuit using an n-p-n transistor



- The input (emitter base) circuit is forward biased.
- $V_{EE}$  is small so so resistance of input circuit is small.
- The output (collector base) circuit is reverse biased  $V_{CC}$  is high voltage battery.  $\therefore$  output resistance is large.

- let 5% of  $I_E$  appear as  $I_B$  due to  $e^-$ -hole combination in base  $\rightarrow$  95% of emitter current flows as  $I_C$ . Due to  $I_C$ ,

$$\text{voltage drop across } R_C = I_C R_C$$


If  $V_C$  is collector voltage (pot. diff. b/w collector & base)

$$\text{then } V_{CB} = V_C + I_C R_C \quad \text{or} \quad V_C = V_{CB} - I_C R_C$$

~~working~~  $\rightarrow$  so when input signal voltage is fed to emitter base circuit, it will change emitter voltage & hence  $I_E$ , which in turn will change  $I_C$ .

Due to this,  $V_C$  will vary. This variation in collector voltage appear as amplified output.

# Transistor as common emitter Amplifier

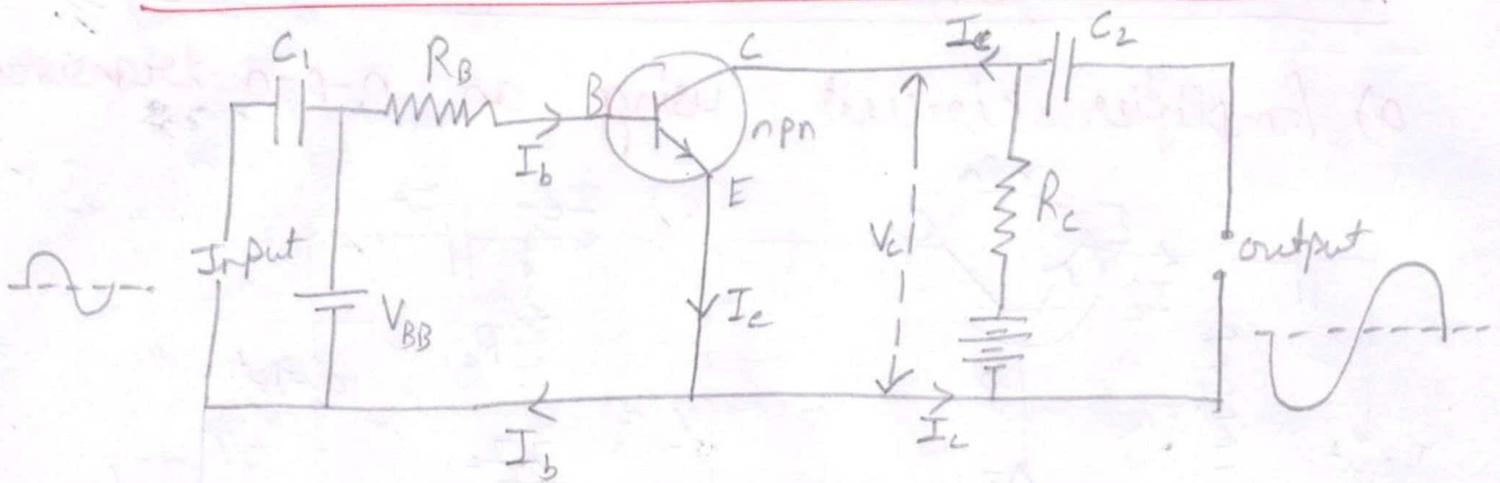

Input circuit is forward biased & output is reversed.  
Resistance of input circuit is low & that of output circuit is high.

- When input signal voltage is feed to Emitter base circuit, it will change emitter voltage & hence  $I_e$ , which inturn will change  $I_c$ .

Due to it collector voltage  $V_c$  will vary in accordance with relation. These variation in voltage appear as amplified output.

\* Phase relation: During +ive half cycle of input a.c. signal voltage, the output signal voltage at collector varies through a negative half cycle & vice-versa.