

Kirchoff's law:-

1. Junction rule:- (Current law)

$$\boxed{\sum I_i = 0}$$


(Algebraic sum of current at a junction)

2. Voltage Rule:-

$$\boxed{\sum V_i = 0}$$

(Around any closed loop)

~~Junction~~
J: ~~4A~~

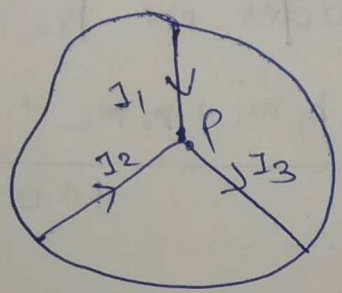


$$\sum I_i = 0$$

At junction point, P


$$\boxed{I_1 + I_2 - I_3 = 0}$$

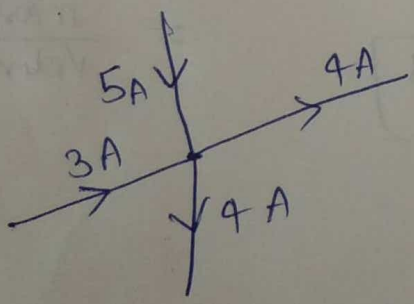Current coming at the junction = +ve
Current going from the junction = -ve



$$\Rightarrow \boxed{5A + 3A - 4A + 4A = 0}$$

Q. $I = ?$

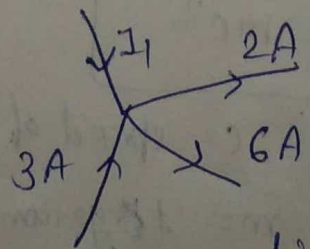

From Current law:-


At junction

$$I_1 + 3 - 2 - 6 = 0$$

$$\boxed{I_1 = \frac{8}{3} \text{ Amp}}$$

→ Voltage Rule: -
for a static field


$$\oint \vec{E} \cdot d\vec{s} = 0$$

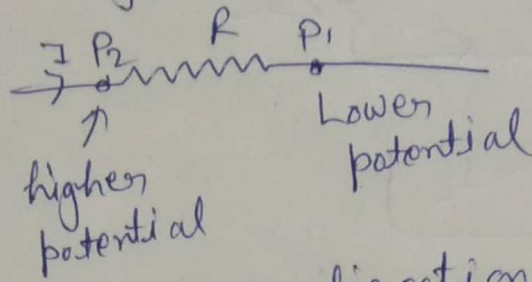

$$V_{P2} > V_{P1}$$


→ Moving in the direction of current
 $\Delta V = \text{negative}$
 $= IR (\text{drop})$

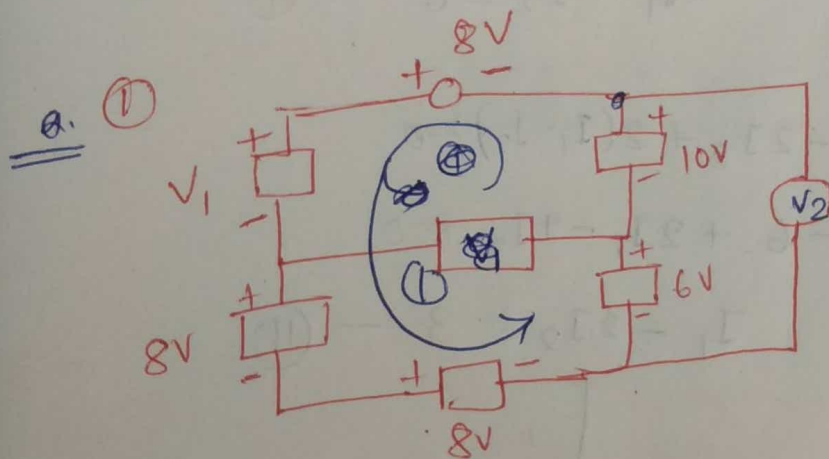Across a battery ΔV is +ve in going from negative to positive terminals.



for loop ①: - $8 - V_1 - 8 + 6 + 10 = 0$

$$V_1 = 8V$$

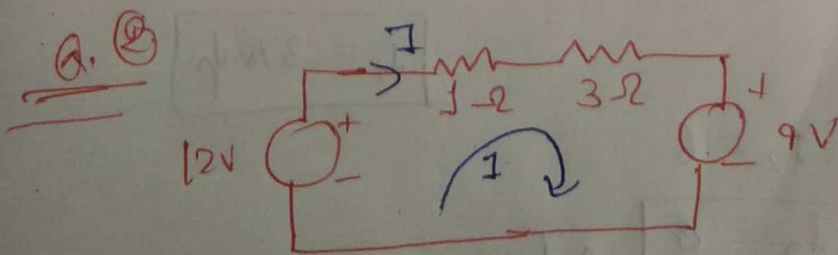


from voltage law: -

$$-I \cdot 1 - I \cdot 3 - 9 + 12$$

$$I = 2 \text{ Amp}$$

Q.3

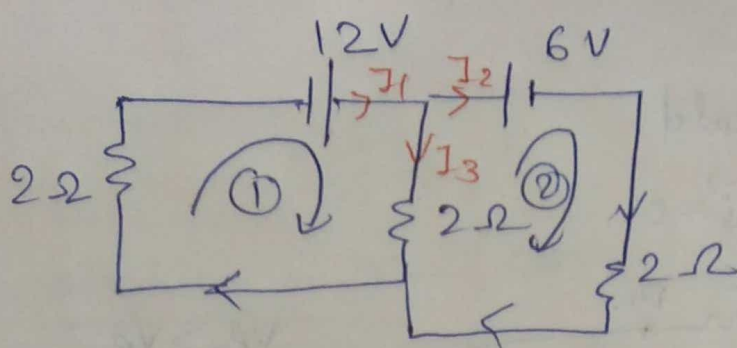

here $I_3 = I_1 - I_2$

I_1 & I_2 are two unknowns

For loop ①:-

$$-2(I_1 - I_2) - 2I_1 + 12 = 0$$

$$-4I_1 + 2I_2 = -12$$

$$2I_1 - I_2 = 6 \quad \text{--- (I)}$$

For loop ②:-

$$-6 - 2I_2 + 2(I_1 - I_2) = 0$$

$$-6 + 2I_1 - 4I_2 = 0$$

$$I_1 - 2I_2 = 3 \quad \text{--- (II)}$$

$$(2I_1 - I_2 = 6) \times 2 \Rightarrow 4I_1 - 2I_2 = 12$$

$$\begin{array}{r} 4I_1 - 2I_2 = 12 \\ I_1 - 2I_2 = 3 \\ \hline 3I_1 = 9 \end{array}$$



$$3I_1 = 9$$

$$I_1 = 3 \text{ Amp}$$

From (I)

$$2 \times 3 - I_2 = 6$$

$$I_2 = 0 \text{ Amp}$$

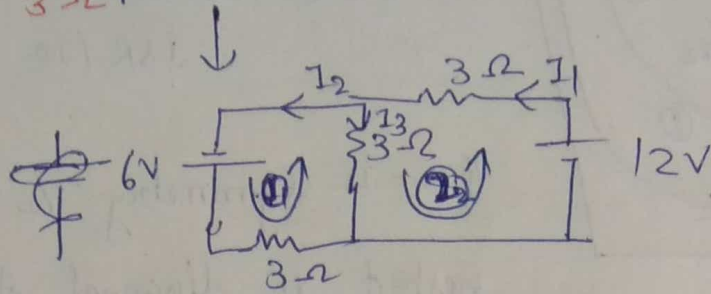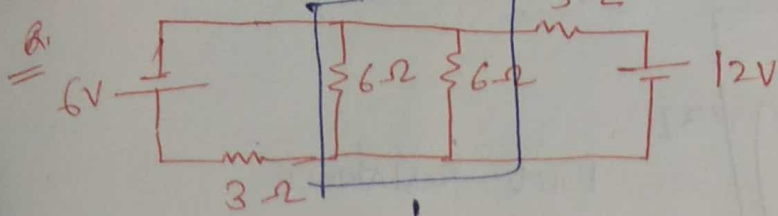

Also $I_3 = I_1 - I_2$

From loop ②: $-3I_1 - 3I_3 + 12 = 0$

$I_1 + I_3 = 4$ — (i)


From loop ①: $-3I_2 - 3I_3 = 6$

$I_2 - I_3 = 2$ — (ii)


$I_2 - I_3 = 2$ — (ii)

Solving we get: $I_1 = \frac{10}{3} \text{ A}$, $I_2 = \frac{8}{3} \text{ A}$

$I_3 = \frac{2}{3} \text{ A}$

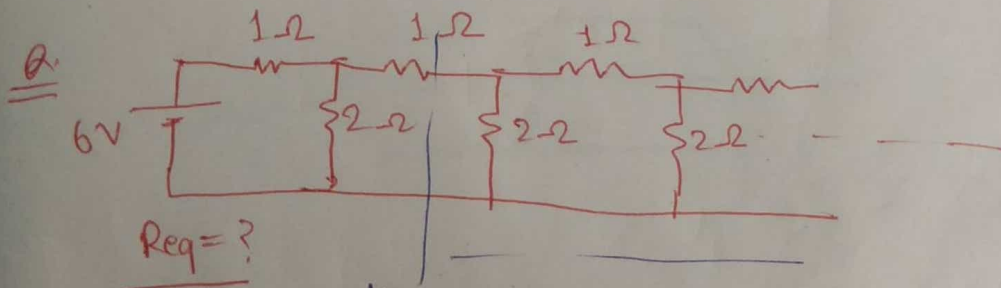

Req = ?

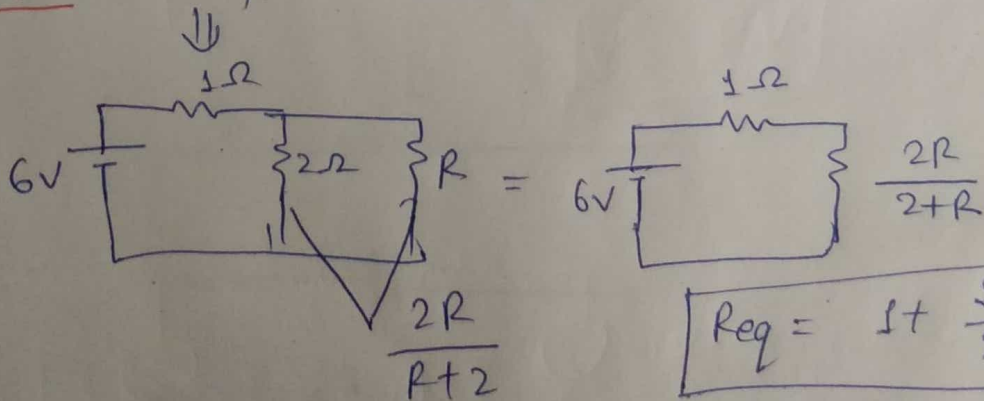


$Req = 1 + \frac{2R}{2+R}$

$Req = R$
 $R = 1 + \frac{2R}{2+R}$

$\Rightarrow R = 2 \Omega$

$\therefore \text{Current} = \frac{6}{1 + \frac{2R}{2+R}}$

$= 3 \text{ A}$

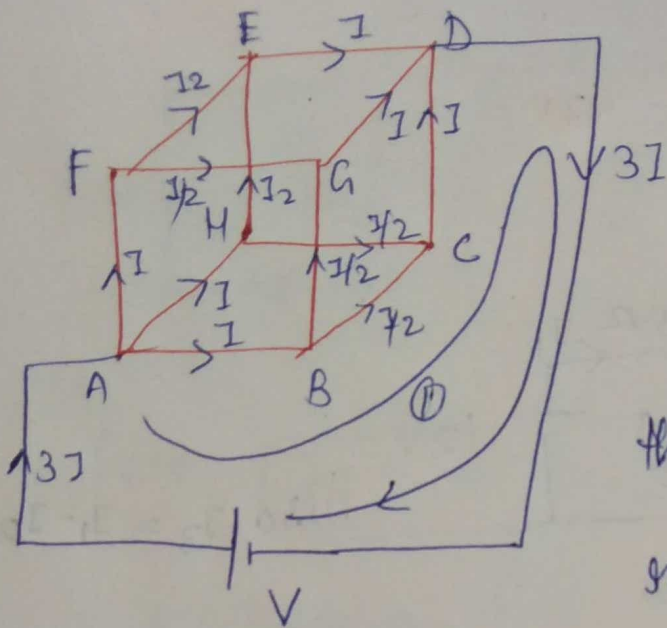

Each Resistance
is R (i.e. each case)

there is symmetry with
respect to diagonal AD .

then current in FE, FG, BG, HC, BC, FH
 $= \frac{I}{2}$

Now loop (1): - $IR + IR + \frac{I}{2}R = V$

$$I = \frac{2}{5} \cdot \frac{V}{R}$$

if $R = 1 \Omega, V = 10V$

then $I = 4A$