

$$I_2 = \frac{n m \epsilon}{nH + mR}$$


$$I_2 = \frac{n m \epsilon}{(\sqrt{nH} - \sqrt{mR})^2 + 2\sqrt{nHmR}}$$

For $I = I_{max}$

$$\Rightarrow \sqrt{nH} = \sqrt{mR}$$


$$R = \frac{nH}{m}$$

$$R = 4\epsilon_2$$

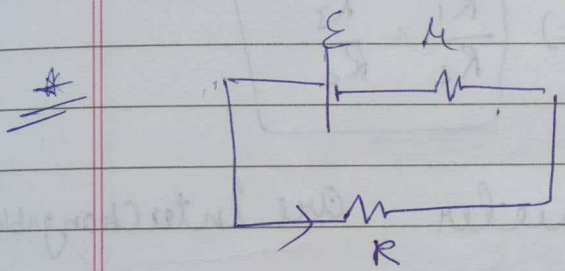


for $I = I_{max}$ or power developed to be Max^m

$$R = H$$

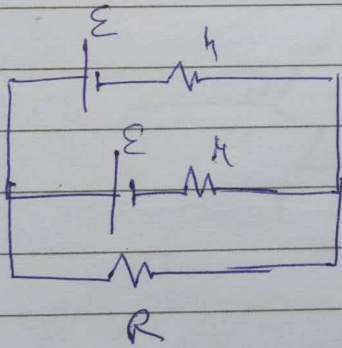

$$R = \frac{H}{2}$$

Wheat stone bridge

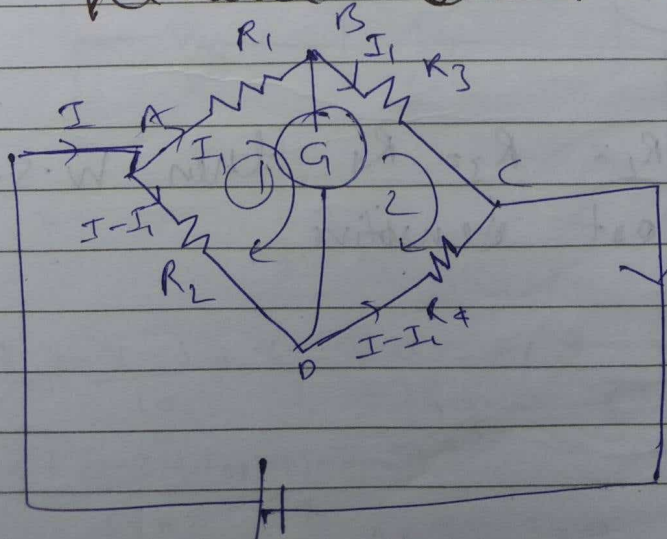

if $V_B = V_D \Rightarrow I_g = 0$
 \Rightarrow Deflection in Galvano. is zero
 \Rightarrow W.S.B is called balanced

loop ① - $-I_1 R_1 + R_2(I - I_1) = 0$

$I_1 R_1 = R_2(I - I_1) \quad \text{--- (I)}$


loop ② - $-I_1 R_3 + (I - I_1) R_4 = 0$

$I_1 R_3 = R_4(I - I_1) \quad \text{--- (II)}$






① \div ②

$\frac{R_1}{R_3} = \frac{R_2}{R_4} \Rightarrow \boxed{\frac{R_1}{R_2} = \frac{R_3}{R_4}}$

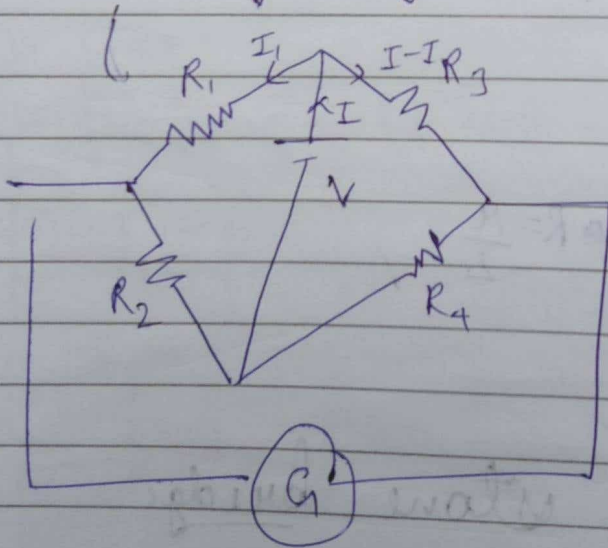→ battery & galvanometer are interchangeable



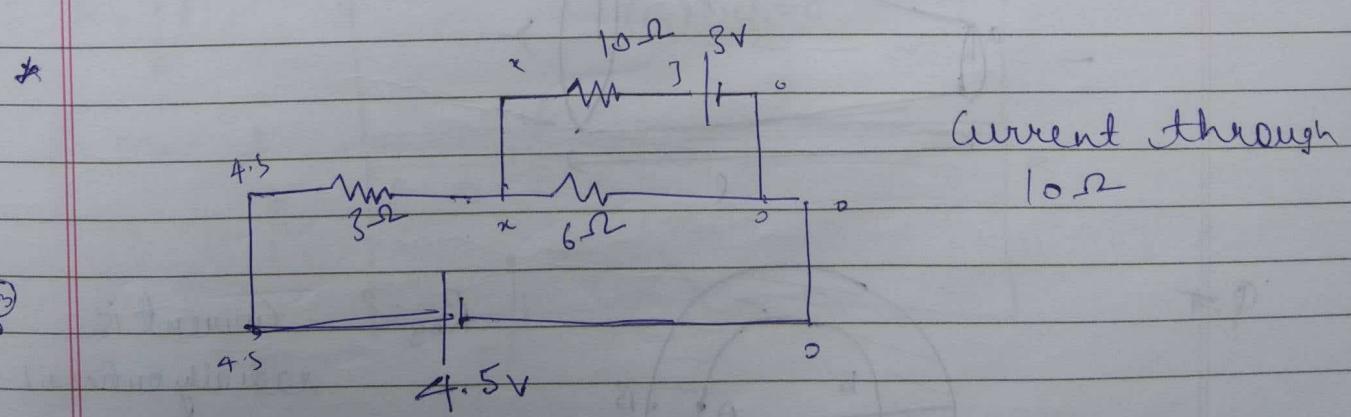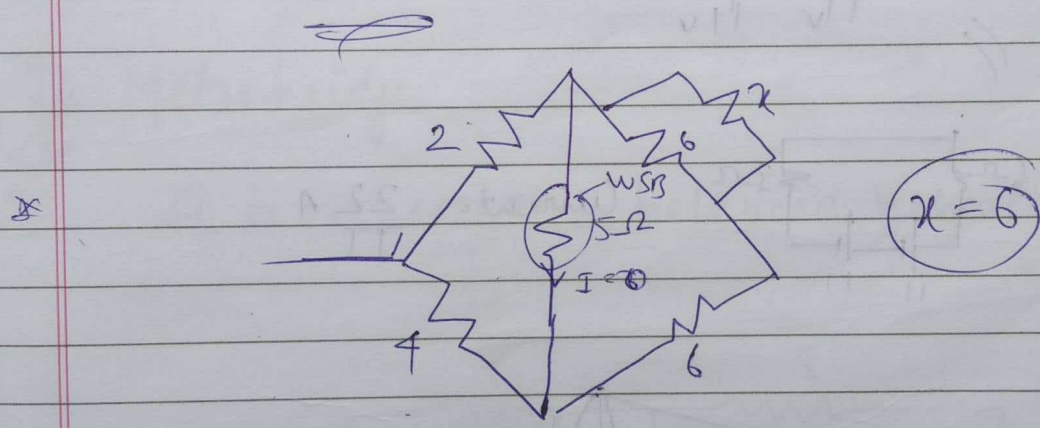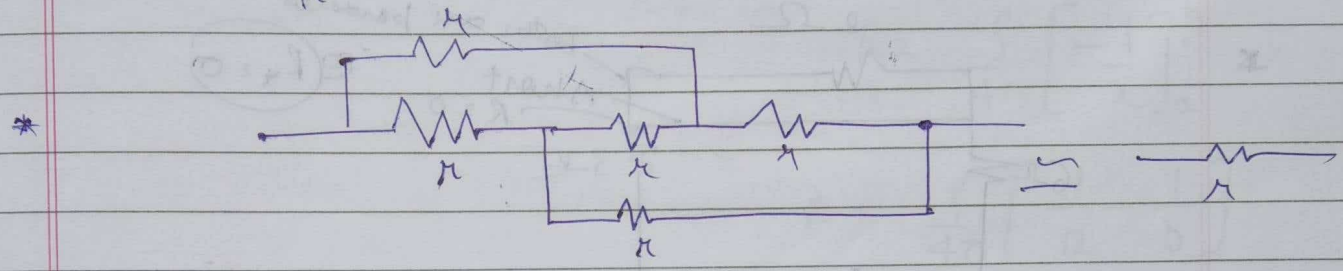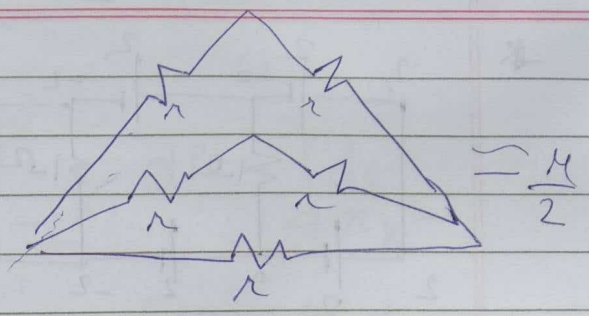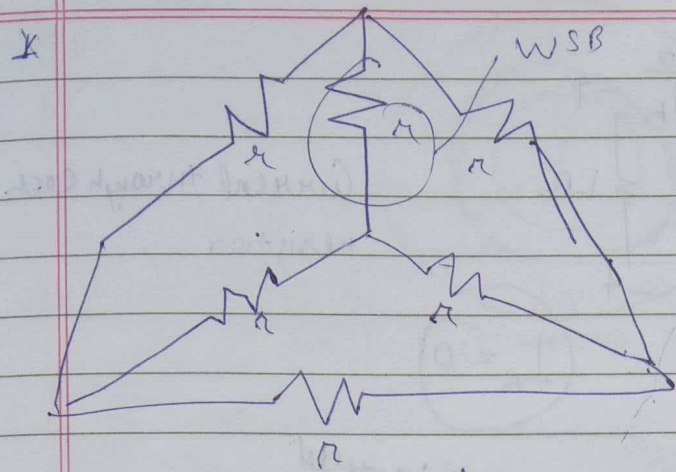→ if $R_1 = R_2 = R_3 = R_4$ then W.S.B is most sensitive



$$\frac{x}{6} + \frac{x-3}{10} + \frac{x-4.5}{3} = 0$$

$$5x + 3x - 9 + 10x - 45 = 0$$

$$18x - 54 = 0 \implies x = 3, I = 0$$

$$(x-4.5)3 + 6x + (x-3)10 = 0$$

$$19x - 13.5 - 30 = 0$$


$$19x = 43.5$$

$$x = 43$$



Meter bridge

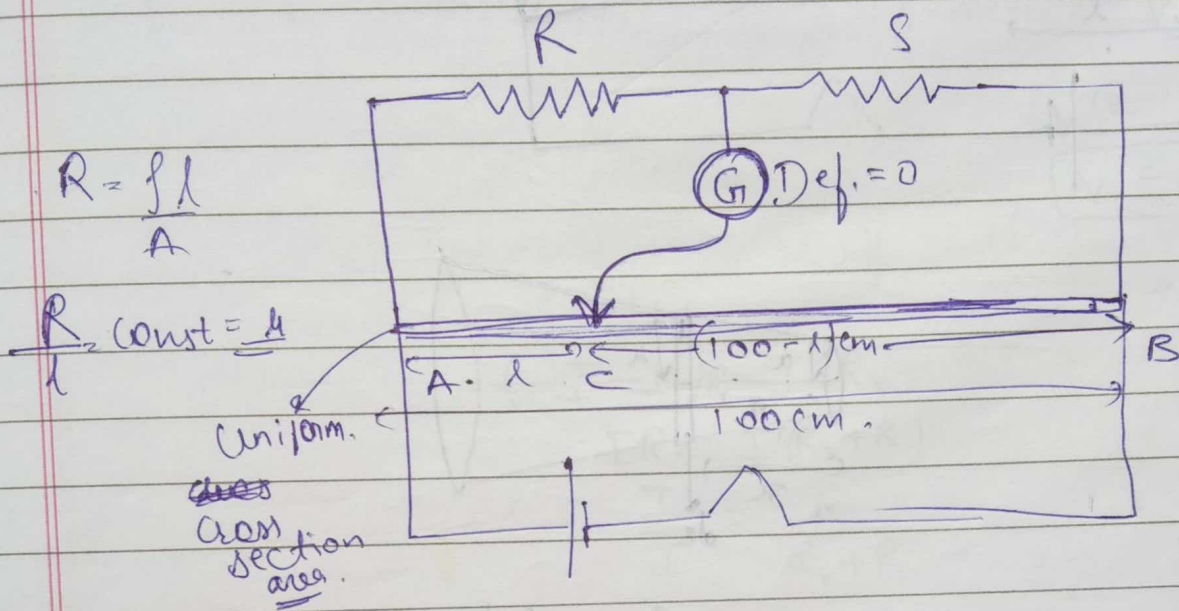It is based on balanced Wheatstone bridge



In balanced condⁿ

$$\frac{R}{R_{AC}} = \frac{S}{R_{CB}}$$



$$\frac{R}{\pi l} = \frac{S}{(100-l) \pi}$$

$$S = \left(\frac{100-l}{l} \right) R$$

Eg- $l = 100 \text{ cm}, R = 100 \Omega, S = ?$

$$S = \left(\frac{100-l}{l} \right) R = \frac{60}{40} \times 100 \Omega = 150 \Omega$$

*

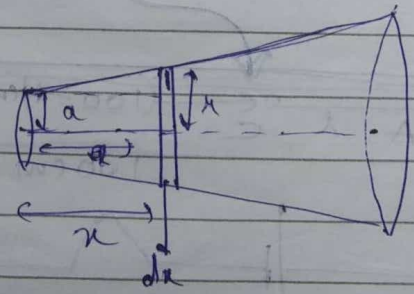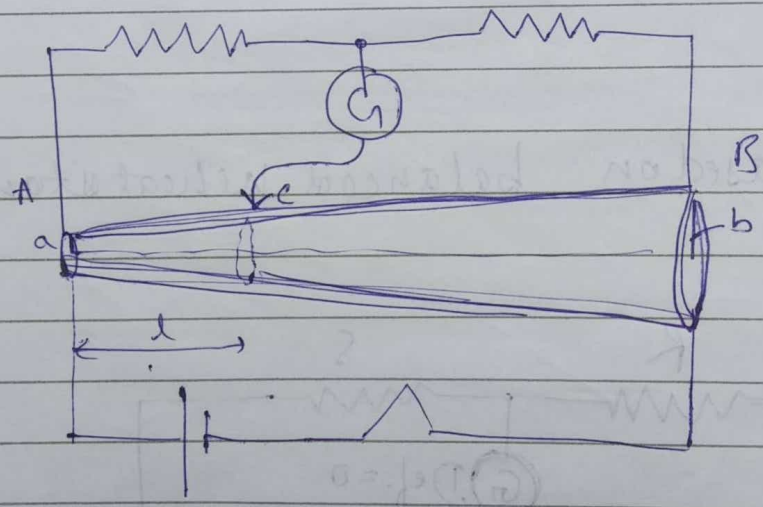


$$dR = \frac{\rho dx}{\pi \left(a + \frac{b-a}{L} x \right)^2}$$

$$R = \int_0^L \frac{\rho dx}{\pi \left(a + \frac{b-a}{L} x \right)^2}$$

$$R_{CB} = \frac{1}{2\pi} \int_0^L \frac{dx}{a + \frac{(b-a)x}{L}}$$

Potentiometer

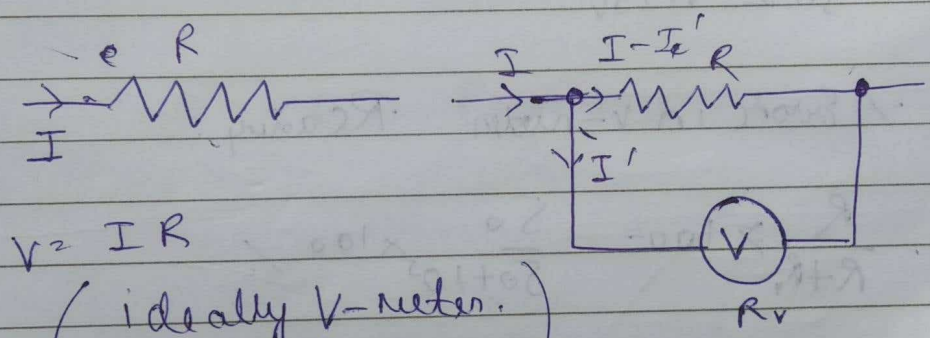- It is used to measure Potential diff. b/w 2 points
- It measures more accurately as compared to the Voltmeter because it does not draw current from the circuit



$V = IR$
 (ideally V-meter.
 $R_v = \infty$
 then $I' = 0$)

Reading of V-meter = $V' = (I - I')R$

$$V' = IR - I'R$$

$$V' = V - I'R$$

also

$$(I - I')R = I'R_v$$

$$IR = I'(R_v + R)$$

$$\frac{I'}{I} = \frac{R}{R_v + R}$$


Error in V-meter reading:
 $V - V'$

$$\% \text{ Error} = \frac{V - V'}{V} \times 100$$

$$\frac{I'R}{IR} \times 100$$

$$\% \text{ Error} = \frac{R}{R+R_v} \times 100$$


Ex 1

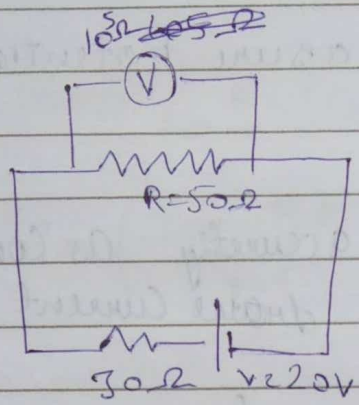

% Error in v-meas Reading

$$\frac{R}{R+R_v} \times 100 = \frac{50}{50+10^5} \times 100 \%$$

* Potentiometer

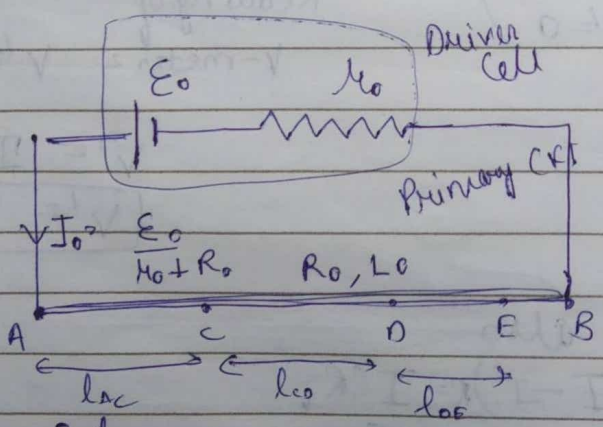

$$R \propto \frac{l}{A}$$

A = const.

$$R \propto l \quad R_{ac} \propto l_{ac}$$

$$R \propto L_0$$

$$R_{ac} = \frac{l_{ac} R_0}{L_0}$$

$$V/m \left(\chi = \frac{I_0 R_0}{L_0} \right) \approx \text{potential gradient}$$

$$V_{AC} = I_0 R_{AC} = \left(\frac{I_0 R_0}{L_0} \right) l_{AC} = \chi l_{AC}$$

$$V_{CO} = I_0 R_{CO} = \left(\frac{I_0 R_0}{L_0} \right) l_{CO}$$


$$V \propto l$$

$$V = \chi l$$

$$V_{OE} = \chi l_{OE}$$



→ L_0 is the length of potential wire.

$R_0 =$ Resistance

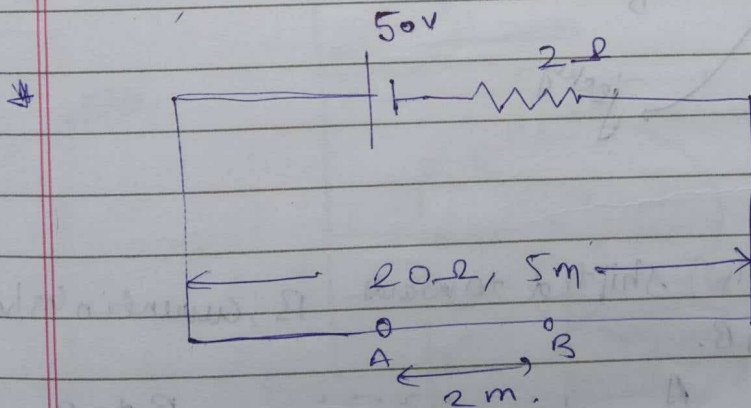


$$I = \frac{50}{2+20} = \frac{50}{22}$$
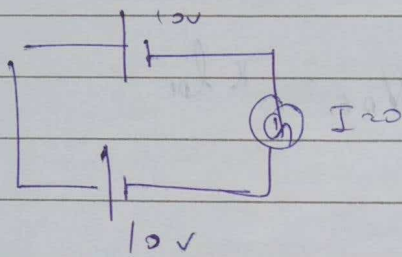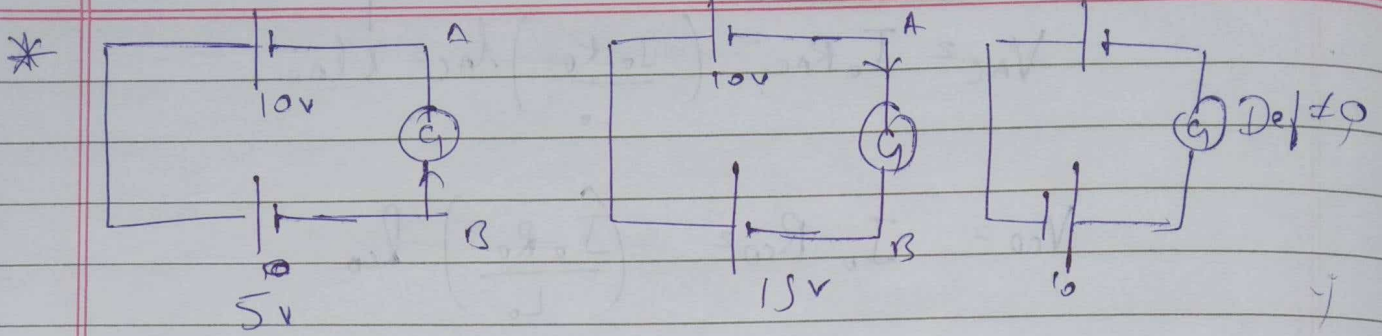
$$V_{AB} = \frac{50}{22} \times \frac{20 \times 2}{8} = \frac{200}{11} \text{ V}$$






Def

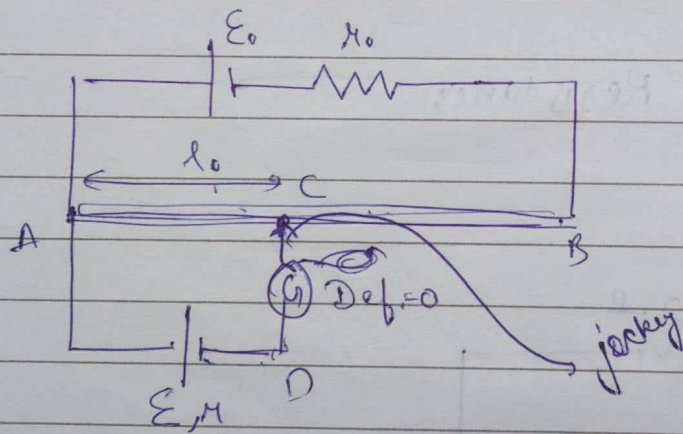

l_0 is balancing length
 $E_1 \propto l_0$

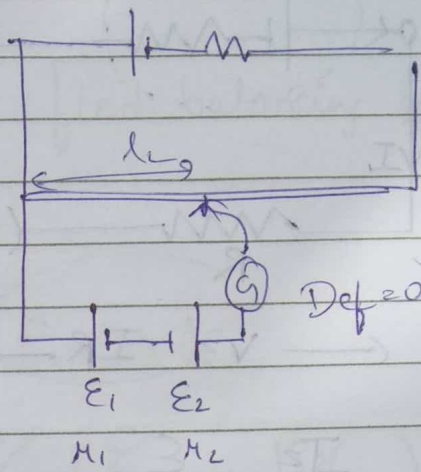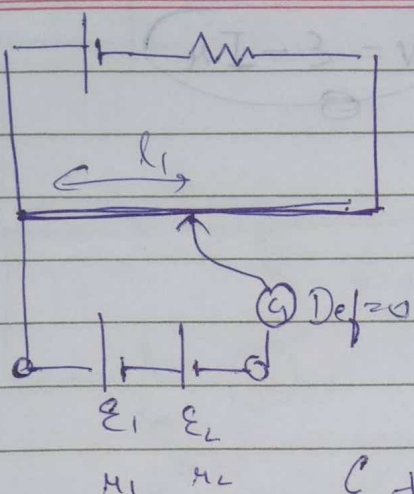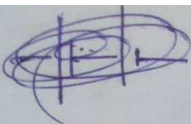- f) When jockey is shifted towards B, current in G is I_{GAB} and is from D to B.
 ii) $I_{GAB} < I_{GAD}$ A, $I_{GAB} > I_{GAD}$ B to D

If $(V_{AB} < E)$ Then E never balance over potentiometer wire.




$$\frac{E_1}{E_2} = \frac{l_1}{l_2}$$

$$E_1 + E_2 = r_1 l_1$$

$$E_1 - E_2 = r_2 l_2$$

Comparison of emf of 2 cells

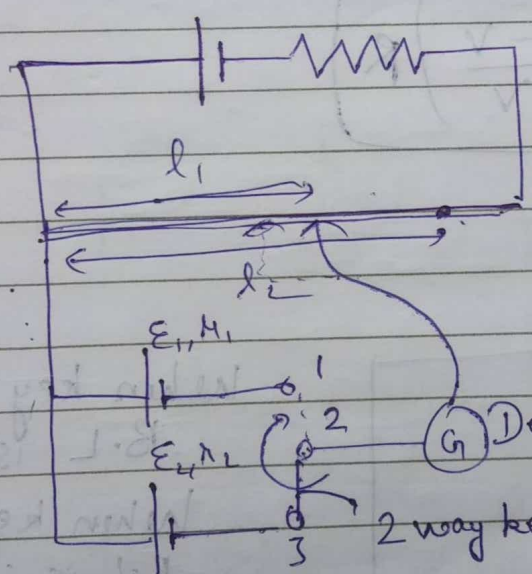

When 1 & 2 are connected of Balance length is l_1 , then $E_1 = r_1 l_1$


if 2 & 3 are ---

... l_2 then $E_2 = r_2 l_2$

$$\frac{E_1}{E_2} = \frac{l_1}{l_2}$$

If $l_1 > l_2$ then $E_1 > E_2$ vice versa

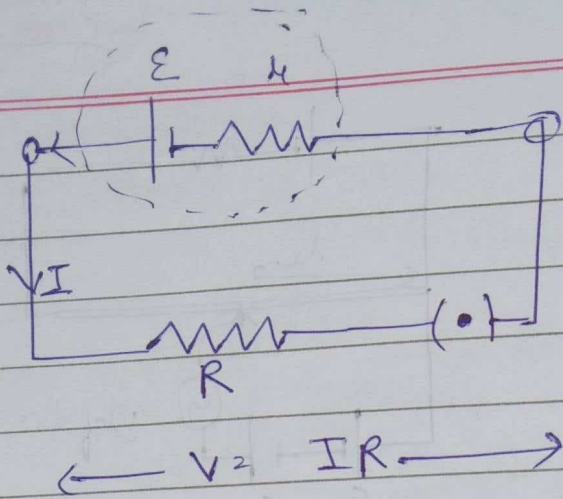Measurement of internal resistance of a cell using potentiometer.



$$V = \varepsilon - I r$$

$$I = \frac{\varepsilon}{r + R}$$


$$I r + I R = \varepsilon$$

$$I r + V = \varepsilon$$

$$r = \frac{\varepsilon - V}{I} \quad \left(I = \frac{V}{R} \right)$$

$$r = \left(\frac{\varepsilon - V}{V} \right) R$$

*

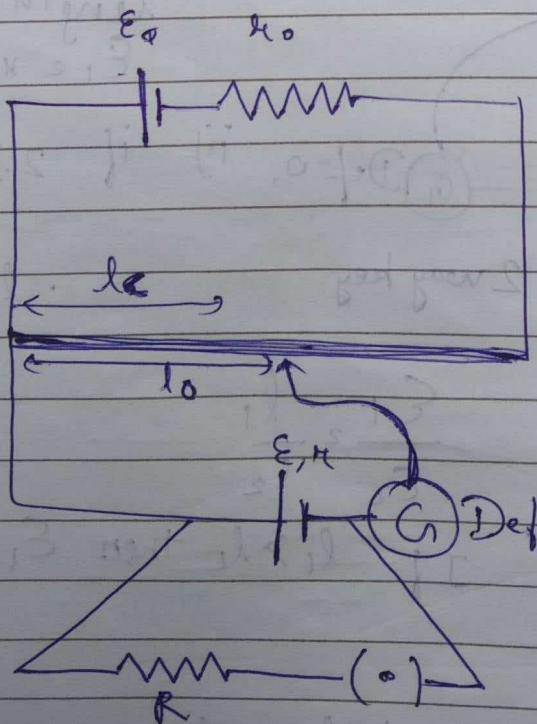


When key is open \downarrow
B.L is l_b then $\varepsilon = x l_b$

When key is closed \downarrow
B.L is l_c then $V = x l_c$

$$\therefore r = \left(\frac{\varepsilon - V}{V} \right) R$$
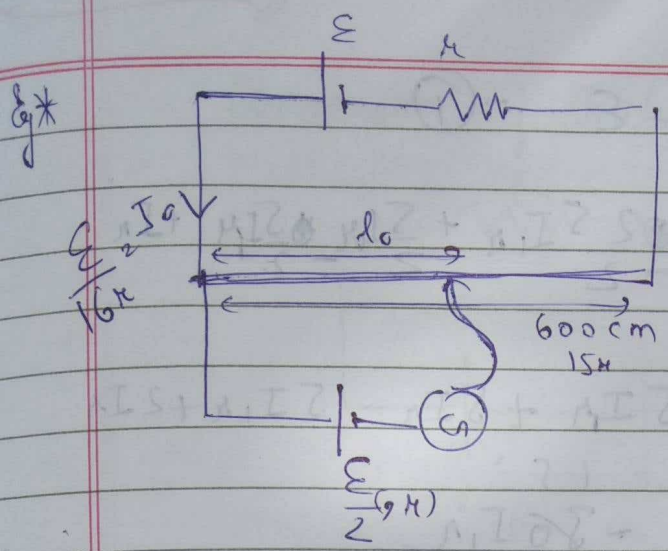
$$r = \left(\frac{l_b - l_c}{l_c} \right) R$$





find balancing length.

$$\epsilon_0 = \frac{\epsilon}{2} \times l_0$$

$$\frac{\epsilon}{2} = \left(\frac{\epsilon}{R + 15\Omega} \times \frac{15\Omega}{600} \right) l_0$$

$$600 \times 16 = l_0 \times 15 \times 2$$

$$320 \text{ cm} = l_0$$

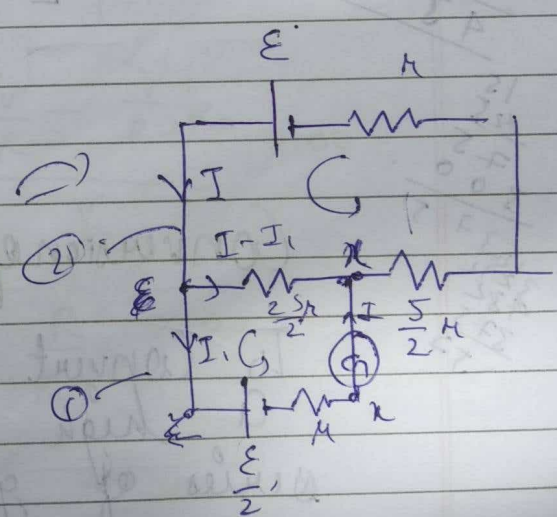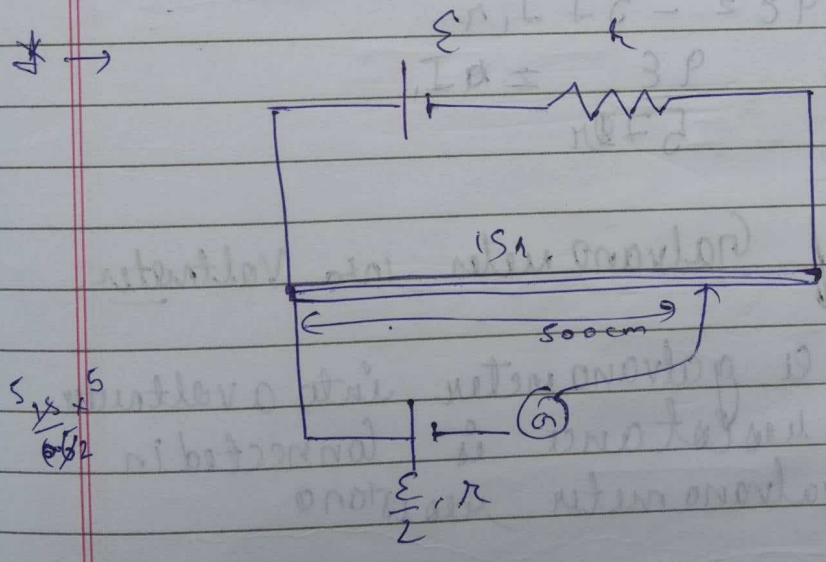

$$\text{loop (1)} \quad -\frac{\epsilon}{2} - I_1 R + (I - I_1) \frac{25\Omega}{2} = 0$$

$$\text{loop (2)} \quad -(I - I_1) \frac{25\Omega}{2} - (I - I_1) \frac{5\Omega}{2} - I R + \frac{\epsilon}{2} = 0$$

$$-\frac{\epsilon}{2} - I_1 R + \frac{25 I_1 \Omega}{2} - \frac{5 I_1 \Omega}{2} = 0$$

$$25I_A - 27I_A = \mathcal{E} \quad \text{--- (1)}$$

$$(2) \quad \mathcal{E} = \frac{25I_A - 25I_A + 5I_A - 5I_A + 2I_A}{2 - 2}$$

$$2\mathcal{E} = \frac{25I_A - 25I_A + 5I_A - 5I_A + 2I_A}{16 - 15}$$

$$2\mathcal{E} = 32I_A - 30I_A$$

$$\mathcal{E} = 16I_A - 15I_A$$

$$\mathcal{E} = 25I_A - 27I_A$$

$$16\mathcal{E} = 400I_A - 432I_A$$


$$25\mathcal{E} = 400I_A - 375I_A$$

$$-9\mathcal{E} = -57I_A$$

$$\frac{9\mathcal{E}}{57} = I_A$$

Conversion of Galvano meter into Voltmeter

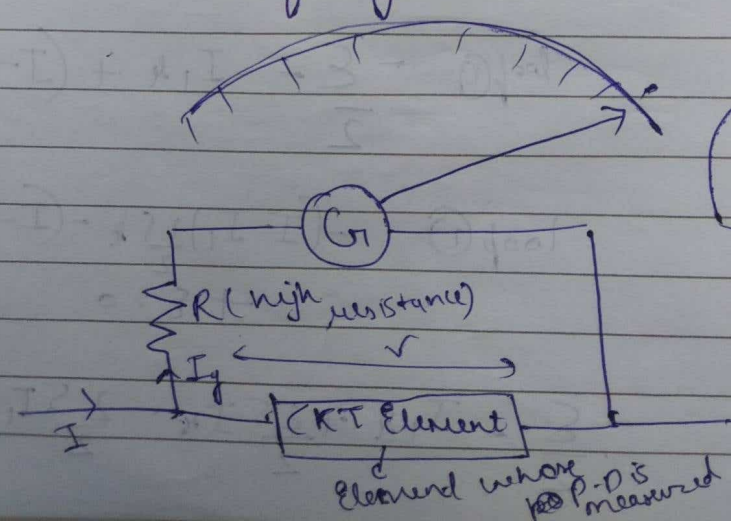To convert a galvano meter into a voltmeter a high resistance is connected in series of galvano meter resistance



$$V = I_g (R + G)$$

full scale Def.
Current = I_g

Voltmeter Resistance = $R + G$

Range of voltmeter = V


$$\begin{array}{r} 25 \\ 16 \overline{) 400} \\ \underline{32} \end{array}$$

$$16$$


$$\begin{array}{r} 25 \\ 16 \overline{) 400} \\ \underline{32} \\ 80 \\ \underline{80} \\ 0 \end{array}$$

$$\begin{array}{r} 15 \\ 57 \overline{) 513} \\ \underline{45} \\ 63 \\ \underline{60} \\ 33 \\ \underline{30} \\ 33 \\ \underline{30} \\ 33 \\ \underline{30} \\ 33 \\ \underline{30} \\ 33 \end{array}$$

Conversion of Galvanometer into Ammeter.

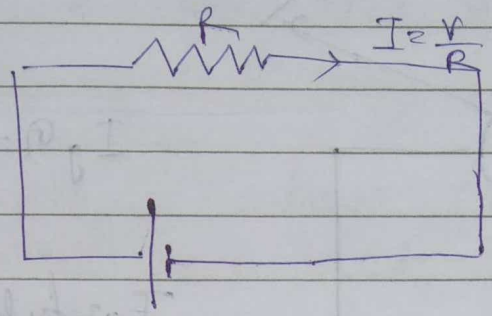

Ideally
 $R_A = 0$

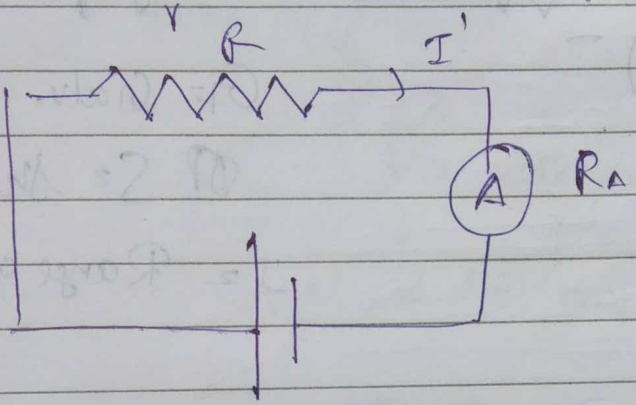

$$I' = \frac{V}{R + R_A}$$

$$\% \text{ Error} = \frac{I - I'}{I} \times 100$$

$$= \frac{\frac{V}{R} - \frac{V}{R + R_A}}{\frac{V}{R}} \times 100$$

$$= \frac{R}{R + R_A} \times 100$$

To convert a Galvanometer into a Ammeter a small resistance is connected in parallel to a Galvanometer which is called shunt.