

Lecture



① parallel plate capacitor:-

we have two plate of same dimension with +ve & -ve charge and arrange in parallel manner.

Let area of plate be

A and separation b/w

them be d.

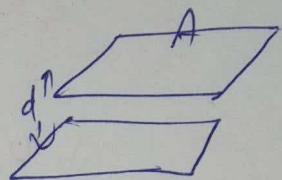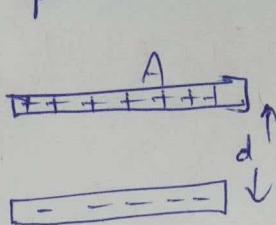


$$\text{then } C = \frac{\epsilon_0 A}{d}$$

ϵ_0 = permittivity
of vacuum.


unit of capacitance = FARAD

$$\text{Also } C = \frac{Q}{V} = \frac{\text{Coulomb}}{\text{Volt}}$$

② cylindrical capacitor:-

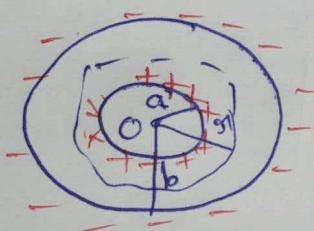

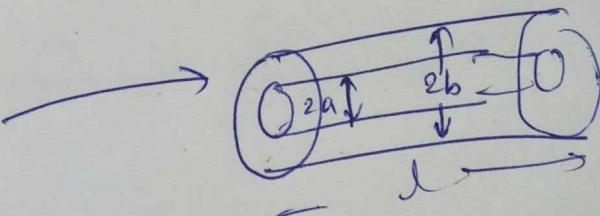Let radius of inner surface be a and outer surface be b.



Let d is charge per unit length
and l is length of cylinder

Let us consider a Gaussian for surface of radius r .

$$\text{then } \text{flux} = \frac{q_{\text{enclosed}}}{\epsilon_0}$$

$$2\pi r \cdot l \cdot E = \frac{Q}{\epsilon_0}$$

$$E = \frac{Q}{2\pi\epsilon_0 r l}$$

now potential diff. $V = V(a) - V(b)$

$$= - \int_b^a E \cdot dr$$

$$= \frac{Q}{2\pi\epsilon_0} \int_a^b \frac{dr}{r}$$

$$V = \frac{Q}{2\pi\epsilon_0} \ln\left(\frac{b}{a}\right)$$

If length is l then

$$l = \frac{Q}{C}$$

$$\therefore V = \frac{Q}{2\pi\epsilon_0 l} \ln\left(\frac{b}{a}\right)$$


$$C = \frac{Q}{V}$$

$$\Rightarrow C = \frac{2\pi\epsilon_0 l}{\ln(b/a)}$$

Capacitance of cylindrical sur.

③ Spherical capacitor:-

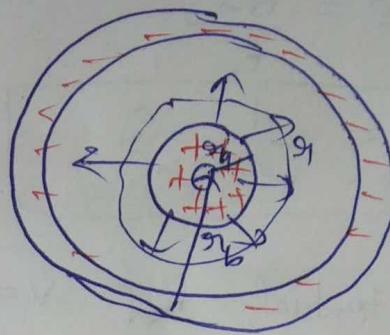Let radius of inner & outer sphere be r_a & r_b resp.



Electric flux through a radius a is

$$= 4\pi r^2 E$$

$$\Rightarrow 4\pi r^2 E = \frac{Q}{\epsilon_0} \quad (\text{Gauss law})$$

$$\boxed{E = \frac{Q}{4\pi\epsilon_0 r^2}}$$

Now potential difference

$$V = - \int_{r_b}^{r_a} \vec{E} \cdot d\vec{s}$$

$$= \int_{r_a}^{r_b} \frac{Q}{4\pi\epsilon_0 r^2} dr$$

$$\boxed{V = \frac{Q}{4\pi\epsilon_0} \left(\frac{1}{r_a} - \frac{1}{r_b} \right)}$$

Now capacitance

$$C = \frac{Q}{V}$$



$$\boxed{C = \frac{4\pi\epsilon_0 (r_a r_b)}{(r_b - r_a)}}$$

limit $r_b \rightarrow \infty$


$$\boxed{C = 4\pi\epsilon_0 r_a}$$

of single sphere.

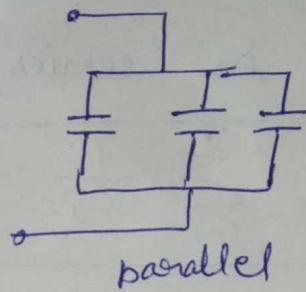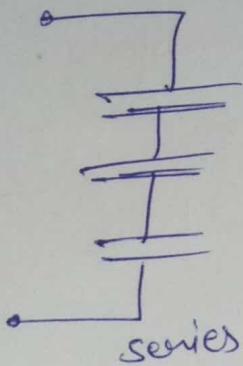Capacitors connected in series & parallel:-



① Series:-

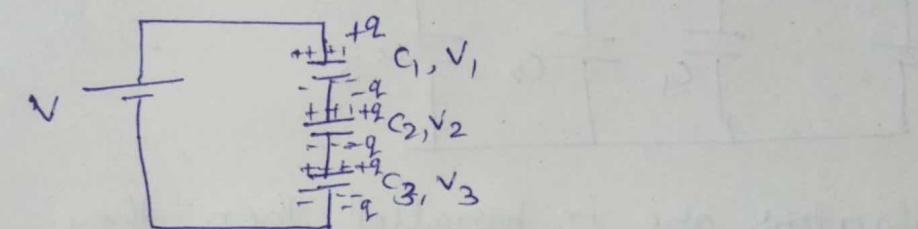

$$V = V_1 + V_2 + V_3$$

∴ Capacitors are in series then charges remain same on each capacitor

Let charge supplied = q

each of capacitor has $+q$ charge

$$\text{then } V_1 = \frac{q}{C_1}, V_2 = \frac{q}{C_2}, V_3 = \frac{q}{C_3}$$

~~$$V = \frac{q}{C_1} + \frac{q}{C_2} + \frac{q}{C_3}$$~~

$$\frac{V}{q} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$


If total capacitance of circuit be C
then $C = \frac{q}{V}$

$$\Rightarrow \frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

for n capacitors in series! —

$$\frac{1}{C} = \sum_{j=1}^n \frac{1}{C_j}$$

(b) Capacitance in parallel:

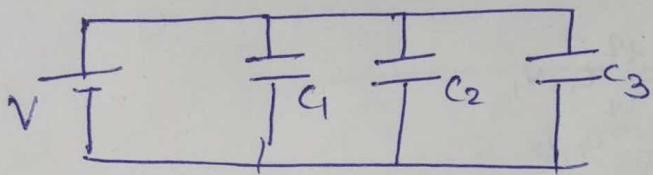

∴ all capacitors are in parallel then they have same voltage and have different charges.

Let Q be the total charge given by battery and q_1, q_2, q_3 be the charges stored in capacitors C_1, C_2, C_3 resp.

$$\text{then } Q = q_1 + q_2 + q_3$$

$$q_1 = C_1 V, \quad q_2 = C_2 V, \quad q_3 = C_3 V$$

$$\therefore Q = C_1 V + C_2 V + C_3 V$$

$$\frac{Q}{V} = C_1 + C_2 + C_3$$

$$C = C_1 + C_2 + C_3$$

for n capacitors in parallel then

$$C = \sum_{j=1}^n C_j$$