

Match List - I with List - II      (JEE MAIN 2021)

	<b>List - I</b>		<b>List - II</b>
(a) $\omega L > \frac{1}{\omega C}$	(i)	Current is in phase with emf	
(b) $\omega L = \frac{1}{\omega C}$	(ii)	Current lags behind the applied emf	
(c) $\omega L < \frac{1}{\omega C}$	(iii)	Maximum current occurs	
(d) Resonant frequency	(iv)	Current leads the emf	

Choose the correct answer from the options given below

- A** a(ii), b(i), c(iv), d(iii)
- B** a(ii), b(i), c(iii), d(iv)
- C** a(iii), b(i), c(iv), d(ii)
- D** a(iv), b(iii), c(ii), d(i)

$$I. (a) \omega L > 1 \Rightarrow X_L > X_C$$

WC

$\Rightarrow$  An inductive circuit

$\Rightarrow$  Current lags the applied emf.

$$(b) \omega L = 1 \Rightarrow X_L = X_C$$

WC

$\Rightarrow$  Current is in phase with emf

$$(c) \omega L < 1 \Rightarrow X_L < X_C$$

WC

$\Rightarrow$  A capacitive circuit

$\Rightarrow$  Current leads the emf

(d) Resonant Resonant frequency:-

We know that current is maximum at resonant frequency.