

A LCR circuit behaves like a damped harmonic oscillator. Comparing it with a physical spring-mass damped oscillator having damping constant 'b', the correct equivalence would be: (JEE MAIN 2020)

- A $L \leftrightarrow k, C \leftrightarrow b, R \leftrightarrow m$
- B $L \leftrightarrow m, C \leftrightarrow k, R \leftrightarrow b$
- C $L \leftrightarrow m, C \leftrightarrow \frac{1}{k}, R \leftrightarrow b$
- D $L \leftrightarrow \frac{1}{b}, C \leftrightarrow \frac{1}{m}, R \leftrightarrow \frac{1}{k}$

For spring-mass damped oscillator

$$ma + bv + kx = 0$$

$$\Rightarrow m \frac{d^2x}{dt^2} + b \frac{dx}{dt} + kx = 0 \quad \text{--- (1)}$$

For LCR circuit

$$L \frac{di}{dt} + iR + \frac{q}{C} = 0$$

$$\Rightarrow L \frac{d^2q}{dt^2} + R \frac{dq}{dt} + \frac{q}{C} = 0 \quad \text{--- (2)}$$

On comparing (1) & (2)

$$L \leftrightarrow m, \quad b \leftrightarrow R, \quad C \leftrightarrow \frac{1}{k}$$