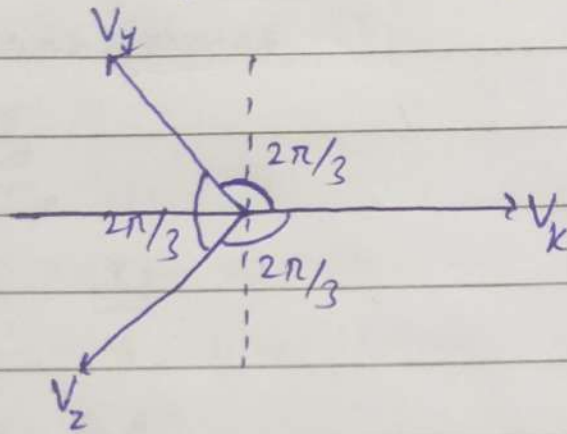


Q. The instantaneous voltages at three terminals marked X, Y and Z are given by $V_x = V_0 \sin \omega t$, $V_Y = V_0 \sin \left(\omega t + \frac{2\pi}{3} \right)$ and $V_Z = V_0 \sin \left(\omega t + \frac{4\pi}{3} \right)$. An ideal voltmeter is configured to read rms value of the potential difference between its terminals. It is connected between points X and Y and then between Y and Z. The reading(s) of the voltmeter will be:- (A) $V_{XY}^{\text{rms}} = V_0$ (B) $V_{YZ}^{\text{rms}} = V_0 \sqrt{\frac{1}{2}}$ (C) Independent of the choice of the two terminals (D) $V_{XY}^{\text{rms}} = V_0 \sqrt{\frac{3}{2}}$ (JEE ADVANCED 2017)

5. Given voltages at terminals X, Y and Z are

$$V_x = V_0 \sin(\omega t) ; V_y = V_0 \sin\left(\omega t + \frac{2\pi}{3}\right) ; V_z = V_0 \sin\left(\omega t + \frac{4\pi}{3}\right)$$

The phasor diagram is as follows:



Amplitude of $V_x = V_y = V_z = V_0$ (Given)

$$\therefore V_{xy} = \sqrt{V_0^2 + V_0^2 - 2(V_0)(V_0) \cos \phi} = (V_x - V_y)$$

(where ϕ is angle between X and Y)

$$\phi = \frac{2\pi}{3}$$

$$\Rightarrow V_{xy} = \sqrt{2V_0^2 - 2V_0^2 \left(-\frac{1}{2}\right)} = (V_x - V_y)$$

$$\Rightarrow V_{xy} = \sqrt{3}V_0$$

$$\therefore V_{xy}(\text{rms}) = \frac{V_{xy}}{\sqrt{2}} = \frac{\sqrt{3}V_0}{\sqrt{2}}$$

Similarly,

$$V_{yz}(\text{rms}) = V_{xz}(\text{rms}) = \frac{\sqrt{3}V_0}{\sqrt{2}}$$

$\Rightarrow \Delta V$ is independent of choice of terminals

Hence, option (C) and (D) are correct