

A fully charged capacitor C with initial charge q_0 is connected to a coil of self inductance L at $t = 0$. The time at which the energy is stored equally between the electric and the magnetic fields is : (JEE MAIN 2011)

A $\frac{\pi}{4}\sqrt{LC}$

B $2\pi\sqrt{LC}$

C \sqrt{LC}

D $\pi\sqrt{LC}$

4. Initial charge on capacitor = q_0

Let time varying charge in given AC-circuit be

$$q = q_0 \sin(\omega t)$$

$$\text{Also, } i = \frac{dq}{dt} \Rightarrow \frac{d[q_0 \sin(\omega t)]}{dt}$$

$$\Rightarrow i = (q_0 \omega) \cos(\omega t)$$

$$\Rightarrow i = i_0 \cos \omega t \quad (\text{where } i_0 = q_0 \omega)$$

Given, magnetic energy = electrostatic energy

$$\Rightarrow \frac{1}{2} L i^2 = \frac{1}{2} \frac{q^2}{C}$$

$$\Rightarrow L [i_0^2 \cos^2(\omega t)] = \frac{q_0^2 \sin^2(\omega t)}{C}$$

$$\Rightarrow (LC) \frac{q_0^2 \omega^2 \cos^2(\omega t)}{\sqrt{LC}} = q_0^2 \sin^2 \omega t$$

(Here, $\omega = \frac{1}{\sqrt{LC}}$ because $X_C = X_L$ at resonant frequency)

$$\Rightarrow \tan^2(\omega t) = 1$$

$$\Rightarrow \omega t = \frac{\pi}{4}$$

$$\Rightarrow \boxed{t = \frac{\pi \sqrt{LC}}{4}}$$