

In an *a. c.* circuit the voltage applied is $E = E_0 \sin \omega t$. The resulting current in the circuit is $I = I_0 \sin \left(\omega t - \frac{\pi}{2} \right)$. The power consumption in the circuit is given by

A $P = \sqrt{2}E_0I_0$

B $P = \frac{E_0I_0}{\sqrt{2}}$

C $P = \text{zero}$

D $P = \frac{E_0I_0}{2}$

Given, $E = E_0 \sin(\omega t)$

$$I = I_0 \sin\left(\omega t - \frac{\pi}{2}\right)$$

$\Delta\phi$ between E and $I \Rightarrow |\Delta\phi| = \left| \omega t - \left(\omega t - \frac{\pi}{2}\right) \right|$

$$|\Delta\phi| = \frac{\pi}{2} \Rightarrow \boxed{\cos\phi = 0}$$

Hence, $P_{\text{consumed}} = \left(\frac{E_0}{\sqrt{2}}\right) \left(\frac{I_0}{\sqrt{2}}\right) \cos\phi$

$$\boxed{P_{\text{consumed}} = 0}$$