

A series LCR circuit driven by 300 V at a frequency of 50 Hz contains a resistance  $R = 3 \text{ k}\Omega$ , an inductor of inductive reactance  $X_L = 250 \pi \Omega$  and an unknown capacitor. The value of capacitance to maximize the average power should be : (Take  $\pi^2 = 10$ ) (JEE MAIN 2021)

- A  $4 \mu\text{F}$
- B  $25 \mu\text{F}$
- C  $400 \mu\text{F}$
- D  $40 \mu\text{F}$

1. In given LCR circuit;

$$V_m = 300V, \quad \nu = 50 \text{ Hz}, \quad R = 3 \text{ k}\Omega, \quad X_L = 250\pi \Omega$$

$$\therefore \omega = 2\pi\nu \Rightarrow 100\pi \text{ rad/s}$$

Let 'C' be the capacitance of required capacitor.

$$\therefore \boxed{X_C = \frac{1}{\omega C} = \frac{1}{(100\pi)C} \Omega} \quad ; \quad \boxed{X_L = 250\pi \Omega}$$

$$\begin{aligned} \therefore Z &= \sqrt{R^2 + (X_C - X_L)^2} \\ &= \sqrt{(3 \times 10^3)^2 + \left[ \frac{1}{(100\pi C)} - (250\pi) \right]^2} \end{aligned}$$

$$\begin{aligned} \therefore P_{av} &= (\frac{\Sigma_{rms}}{\sqrt{2}}) (\frac{I_{rms}}{\sqrt{2}}) \cos \phi \\ &= \left( \frac{\Sigma_0}{\sqrt{2}} \right) \left( \frac{I_0}{\sqrt{2}} \right) \frac{R}{Z} \quad \left( \because \cos \phi = \frac{R}{Z} \right) \end{aligned}$$

$$= \left( \frac{\Sigma_0}{\sqrt{2}} \right) \left( \frac{\Sigma_0}{\sqrt{2} Z} \right) \frac{R}{Z}$$

$$P_{av} = \frac{\Sigma_0^2 R}{2Z^2}$$

(★ Trick :- No need to evaluate whole expression. Just take derivative w.r.t. C and evaluate it.)

$$\text{As } P_{av} \propto \frac{1}{Z^2}$$

$\Rightarrow$  For  $P_{av}$  to be max.,  $Z^2$  must be minimum

$$\Rightarrow Z^2 = (3 \times 10^3)^2 + \left( \frac{1}{100\pi C} - 250\pi \right)^2 \text{ is minimum}$$

which is possible only when  $X_C - X_L = 0$

i.e.  $\frac{1}{100\pi C} - 250\pi = 0$

$$\frac{1}{100\pi C}$$

$$\Rightarrow C = \frac{1}{(100\pi)(250\pi)}$$

$$\Rightarrow C = \frac{1}{25 \times 10^3 \times 10}$$

(Taking  $\pi^2 = 10$ )

$$\Rightarrow \boxed{C = 4 \mu F}$$