

An AC source rated 100 V (rms) supplies a current of 10 A (rms) to a circuit. The average power delivered by the source

- (a) must be 1000 W
- (b) may be 1000 W
- (c) may be greater than 1000 W
- (d) may be less than 1000 W

In the given AC source

$$E_{\text{rms}} = 100 \text{ V}, \quad I_{\text{rms}} = 10 \text{ A}$$

$$\begin{aligned} \therefore P_{\text{average}} &= (E_{\text{rms}})(I_{\text{rms}}) \cos \phi \\ &= (100)(10) \cos \phi \\ &= 1000 \cos \phi \end{aligned}$$

{ As  $\cos \phi$  can lie between 0 to 1 (inclusively) }  
i.e.  $0 \leq \cos \phi \leq 1$

$$\Rightarrow P_{\text{average}} \leq 1000 \text{ W}$$

It can be 1000W or less than 1000W

Hence, option (b) and (d) are correct.