

Q1: A series AC circuit containing an inductor (20 mH), a capacitor (120 F) and a resistor (60 Ω) is driven by an AC source of 24 V/50 Hz. The energy dissipated in the circuit in 60 s is

- (a) 3.39×10^3 J
- (b) 5.65×10^2 J
- (c) 2.26×10^3 J
- (d) 5.17×10^2 J

5. In given AC circuit,

$$L = 20 \text{ mH} = 20 \times 10^{-3} \text{ H}$$

$$C = 120 \text{ nF} \quad (\text{C is written in F \& not } \mu\text{F by mistake})$$

$$R = 60 \Omega$$

$$\text{AC source is } (24 \text{ V} / 50 \text{ Hz}) \Rightarrow \frac{V}{\text{rms}} = 24 \text{ V}, \nu = 50 \text{ Hz}$$

$$\Rightarrow \omega = 2\pi\nu$$

$$= 2\pi(50) \Rightarrow 100\pi \text{ rad/s}$$

$$\therefore X_C = \frac{1}{\omega C} \Rightarrow \frac{1}{100\pi(120 \times 10^{-9})} \Rightarrow 10^3 \Omega$$

$$\omega C = (100\pi)(120 \times 10^{-9}) = 12\pi \times 10^{-3}$$

$$X_L = \omega L \Rightarrow (100\pi)(20 \times 10^{-3}) \Rightarrow 2\pi \Omega$$

$$\Rightarrow (X_C - X_L)^2 = \left(\frac{10^3}{12\pi \times 10^{-3}} - 2\pi \right)^2 \Omega$$

$$= 410 \Omega^2$$

$$\begin{aligned}\therefore Z^2 &= R^2 + (X_C - X_L)^2 \\ &= (60)^2 + (410)^2\end{aligned}$$

$$\boxed{Z^2 = 4010 \Omega^2}$$

$$\begin{aligned}\therefore P_{av} \text{ dissipated} &= (E_{rms})(I_{rms}) \cos \phi \\ &= (E_{rms}) \left(\frac{E_{rms}}{Z} \right) \left(\frac{R}{Z} \right) \quad \left(\because \cos \phi = \frac{R}{Z} \right) \\ &= \frac{E_{rms}^2 R}{Z^2} \\ &= \frac{(24)^2 (60)}{(4010)} \\ &= 8.62 \text{ W}\end{aligned}$$

$$\begin{aligned}\therefore \text{Energy dissipated} &= (P_{av} \text{ dissipated}) \times \text{time} \\ &= 8.62 \times 60 \quad (\because t = 60 \text{ s given}) \\ &= 517 \text{ J}\end{aligned}$$