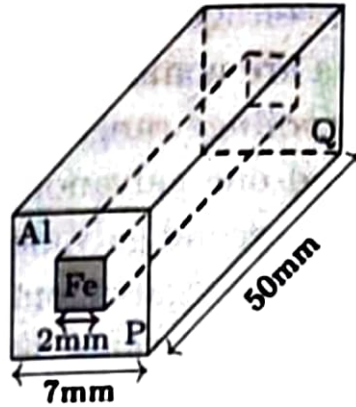


Q. 11 In an aluminium (Al) bar of square cross-section, a square hole is drilled and is filled with iron (Fe) as shown in the figure. The electrical resistivities of Al and Fe are  $2.7 \times 10^{-8} \Omega \text{ m}$  and  $1.0 \times 10^{-7} \Omega \text{ m}$ , respectively. The electrical resistance between the two faces P and Q of the composite bar is (2015)



- (A)  $\frac{2475}{64} \mu\Omega$  (B)  $\frac{1875}{64} \mu\Omega$  (C)  $\frac{1875}{49} \mu\Omega$  (D)  $\frac{2475}{132} \mu\Omega$

**Sol.** The resistance of a conductor of length  $l$ , cross-sectional area  $A$ , and material resistivity  $\rho$  is given by  $R = \rho l/A$ . For iron bar, length is  $l_{\text{Fe}} = 5 \times 10^{-2} \text{ m}$ , cross-sectional area is  $A_{\text{Fe}} = (2 \times 10^{-3})^2 = 4 \times 10^{-6} \text{ m}^2$ , and resistivity is  $\rho_{\text{Fe}} = 1.0 \times 10^{-7} \Omega \text{ m}$ .

The resistance of the iron bar is

$$R_{\text{Fe}} = \frac{\rho_{\text{Fe}} l_{\text{Fe}}}{A_{\text{Fe}}} = \frac{(1 \times 10^{-7})(5 \times 10^{-2})}{4 \times 10^{-6}} = 1250 \mu\Omega.$$

For the aluminium bar,  $A_{\text{Al}} = (7 \times 10^{-3})^2 - (2 \times 10^{-3})^2 = 4.5 \times 10^{-5} \text{ m}^2$ ,  $l_{\text{Al}} = 5 \times 10^{-2} \text{ m}$ , and  $\rho_{\text{Al}} = 2.7 \times 10^{-8} \Omega \text{ m}$ . The resistance of the aluminium bar is

$$R_{\text{Al}} = \frac{\rho_{\text{Al}} l_{\text{Al}}}{A_{\text{Al}}} = \frac{(2.7 \times 10^{-8})(5 \times 10^{-2})}{4.5 \times 10^{-5}} = 30 \mu\Omega.$$

The iron and aluminium bars are connected in parallel between P and Q. Thus, the equivalent resistance of the composite bar is

$$\begin{aligned} R_{\text{eq}} &= R_{\text{Fe}} \parallel R_{\text{Al}} = \frac{R_{\text{Fe}} R_{\text{Al}}}{R_{\text{Fe}} + R_{\text{Al}}} = \frac{(1250)(30)}{1250 + 30} \\ &= \frac{1875}{64} \mu\Omega. \end{aligned}$$

Ans. B  $\square$