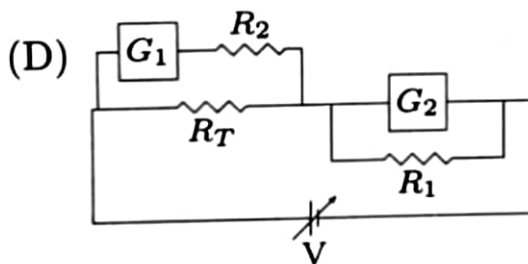
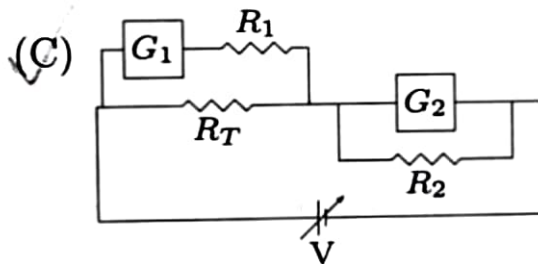
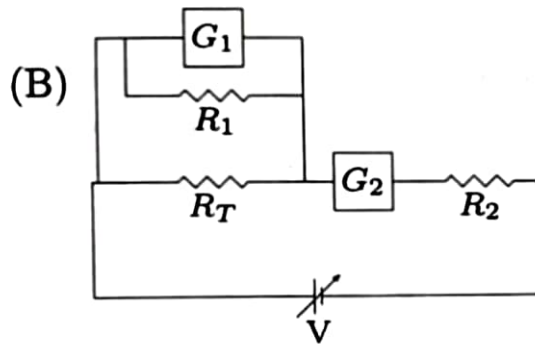
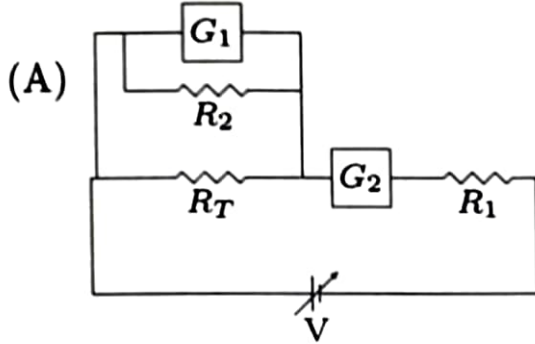


Q.09 To verify Ohm's law, a student is provided with a test resistor  $R_T$ , a high resistance  $R_1$ , and a small resistance  $R_2$ , two identical galvanometers  $G_1$  and  $G_2$ , and a variable voltage source  $V$ . The correct circuit to carry out the experiment is (2010)



**Sol.** To verify Ohm's law, we need to measure the voltage across the test resistance  $R_T$  and current passing through it. The voltage can be measured by connecting a high resistance  $R_1$  in series with galvanometer. This combination becomes a voltmeter and should be connected in parallel to  $R_T$ . The current can be measured by connecting a low resistance  $R_2$  (shunt) in parallel with galvanometer. This combination becomes an ammeter and should be connected in series to measure the current through  $R_T$ .

Ans. C  $\square$