

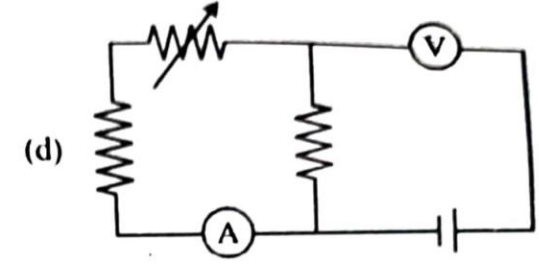
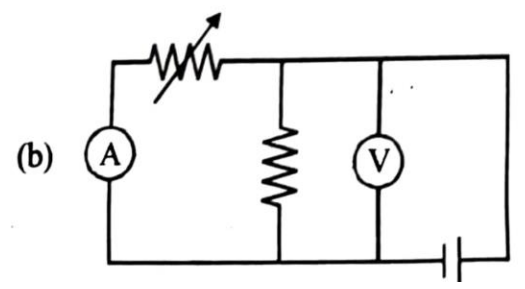


Q. 03 Correct set up to verify Ohm's law is :

[Online April 23, 2013]

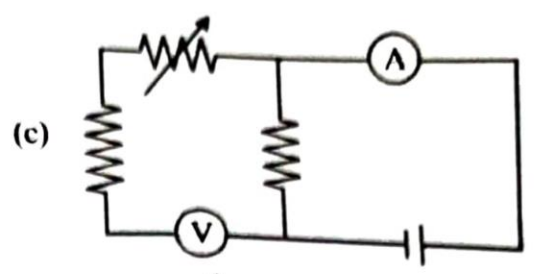

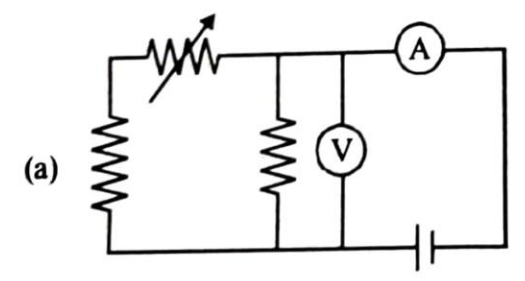03 (a) In ohm's law, we check  $V = IR$  where  $I$  is the current flowing through a resistor and  $V$  is the potential difference across that resistor. Only option (a) fits the above criteria. Remember that ammeter is connected in series with resistance and voltmeter parallel with the resistance.

