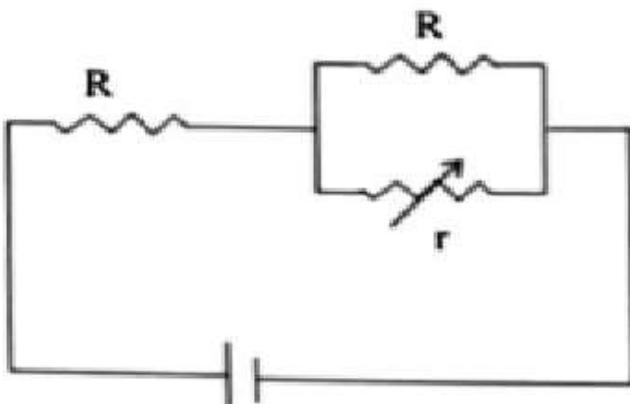


Q 03



In the circuit shown, the resistance  $r$  is a variable resistance. If for  $r = fR$ , the heat generation in  $r$  is maximum then the value of  $f$  is : [Online April 9, 2016]