

Q 08 Two electric bulbs rated $25\text{W} - 220\text{V}$ and $100\text{W} - 220\text{V}$ are connected in series to a 440V supply. Which of the bulbs will fuse? [2012]


- (a) Both (b) 100W (c) 25W (d) Neither

(c) The current upto which bulb rated $25\text{W} - 220\text{V}$, will not fuse

$$I_1 = \frac{W_1}{V_1} = \frac{25}{220} \text{ Amp}$$

$$\text{Similarly, } I_2 = \frac{W_2}{V_2} = \frac{100}{220} \text{ Amp}$$

The current flowing through the circuit

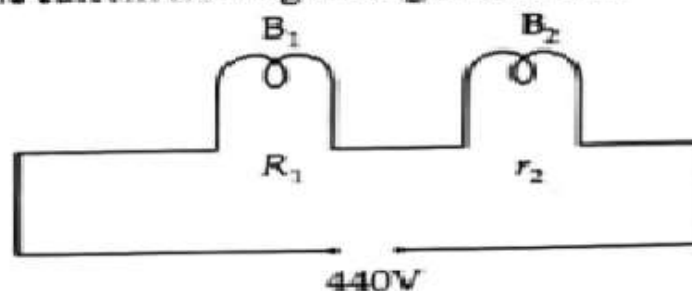

$$I = \frac{440}{R_{\text{eff}}}$$

$$R_{\text{eff}} = R_1 + R_2$$

$$R_1 = \frac{V_1^2}{P_1} = \frac{(220)^2}{25} ; R_2 = \frac{V_2^2}{P} = \frac{(220)^2}{100}$$

$$I = \frac{440}{\frac{(220)^2}{25} + \frac{(220)^2}{100}}$$

$$= \frac{440}{(220)^2 \left[\frac{1}{25} + \frac{1}{100} \right]}$$

$$I = \frac{40}{220} \text{ Amp}$$

$$\therefore I_1 \left(= \frac{25}{220} \text{ A} \right) < I \left(= \frac{40}{220} \text{ A} \right) < I_2 \left(= \frac{100}{220} \text{ A} \right)$$

Thus the bulb rated $25\text{W} - 220\text{V}$ will fuse.