

Q 10

Three resistors of $4\ \Omega$, $6\ \Omega$ and $12\ \Omega$ are connected in parallel and the combination is connected in series with a $1.5\ \text{V}$ battery of $1\ \Omega$ internal resistance. The rate of Joule heating in the $4\ \Omega$ resistor is [Online May 12, 2012]

(a) $0.55\ \text{W}$ (b) $0.33\ \text{W}$ (c) $0.25\ \text{W}$ (d) $0.86\ \text{W}$

- (c) Resistors $4\ \Omega$, $6\ \Omega$ and $12\ \Omega$ are connected in parallel, its equivalent resistance (R) is given by

$$\frac{1}{R} = \frac{1}{4} + \frac{1}{6} + \frac{1}{12} \Rightarrow R = \frac{12}{6} = 2\ \Omega$$

Again R is connected to $1.5\ \text{V}$ battery whose internal resistance $r = 1\ \Omega$.

Equivalent resistance now,

$$R' = 2\ \Omega + 1\ \Omega = 3\ \Omega$$

$$\text{Current, } I_{\text{total}} = \frac{V}{R'} = \frac{1.5}{3} = \frac{1}{2}\ \text{A}$$

$$I_{\text{total}} = \frac{1}{2} = 3x + 2x + x = 6x$$

$$\Rightarrow x = \frac{1}{12}$$

$$\therefore \text{Current through } 4\ \Omega \text{ resistor} = 3x$$

$$= 3 \times \frac{1}{12} = \frac{1}{4}\ \text{A}$$

Therefore, rate of Joule heating in the $4\ \Omega$ resistor

$$= I^2 R = \left(\frac{1}{4}\right)^2 \times 4 = \frac{1}{4} = 0.25\ \text{W}$$