

## Question 03

**(c)** A low voltage supply from which one needs high currents must have very low internal resistance. Why?

## Answer 03

**(c)** According to Ohm's law, the relation for the potential is  $V = IR$

Voltage ( $V$ ) is directly proportional to current ( $I$ ).

$R$  is the internal resistance of the source.

$$I = \frac{V}{R}$$

If  $V$  is low, then  $R$  must be very low, so that high current can be drawn from the source.