

Q 17 A 220 volt, 1000 watt bulb is connected across a 110 volt mains supply. The power consumed will be [2003]

- (a) 750 watt
- (b) 500 watt
- (c) 250 watt
- (d) 1000 watt

(c) We know that $R = \frac{V_{\text{rated}}^2}{P_{\text{rated}}} = \frac{(220)^2}{1000}$

When this bulb is connected to 110 volt mains supply we get

$$P = \frac{V^2}{R} = \frac{(110)^2 \times 1000}{(220)^2} = \frac{1000}{4} = 250 \text{ W}$$