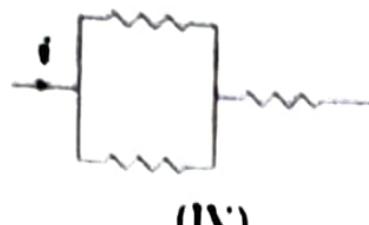
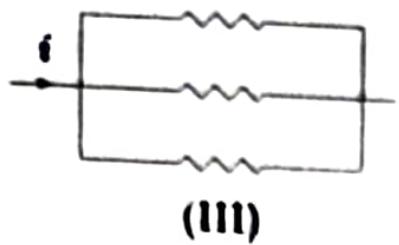
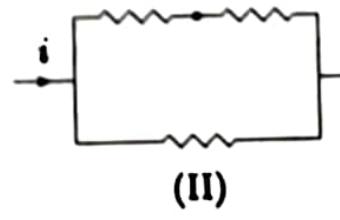
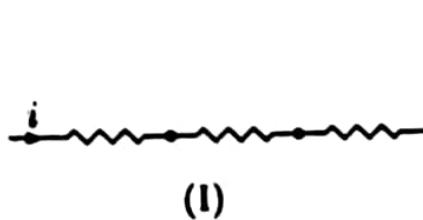


**Q 20.** The three resistances of equal value are arranged in the different combination shown below. Arrange them in increasing order of power dissipation. (2003)



- (A) III < II < IV < I    (B) II < III < IV < I  
 (C) I < IV < III < II    (D) I < III < II < IV

**Sol.** The equivalent resistances and power dissipation of the given combination are given by

$$R_I = R + R + R = 3R, \quad P_I = i^2 R_I = 3i^2 R,$$

$$R_{II} = (R + R) \parallel R = \frac{2}{3}R, \quad P_{II} = i^2 R_{II} = \frac{2}{3}i^2 R,$$

$$R_{III} = R \parallel R \parallel R = \frac{1}{3}R, \quad P_{III} = i^2 R_{III} = \frac{1}{3}i^2 R,$$

$$R_{IV} = (R \parallel R) + R = \frac{3}{2}R, \quad P_{IV} = i^2 R_{IV} = \frac{3}{2}i^2 R.$$

*Ans.* A