

## Q. 02

A storage battery of emf 8.0 V and internal resistance 0.5  $\Omega$  is being charged by a 120 V dc supply using a series resistor of 15.5  $\Omega$ . What is the terminal voltage of the battery during charging? What is the purpose of having a series resistor in the charging circuit?

Answer

---

Emf of the storage battery,  $E = 8.0$  V

Internal resistance of the battery,  $r = 0.5$   $\Omega$

DC supply voltage,  $V = 120$  V

Resistance of the resistor,  $R = 15.5$   $\Omega$

Effective voltage in the circuit =  $V^1$

$R$  is connected to the storage battery in series. Hence, it can be written as

$$V^1 = V - E$$

$$V^1 = 120 - 8 = 112$$
 V

Current flowing in the circuit =  $I$ , which is given by the relation,

$$I = \frac{V^1}{R+r}$$
$$= \frac{112}{15.5+0.5} = \frac{112}{16} = 7$$
 A

Voltage across resistor  $R$  given by the product,  $IR = 7 \times 15.5 = 108.5$  V

DC supply voltage = Terminal voltage of battery + Voltage drop across  $R$

Terminal voltage of battery =  $120 - 108.5 = 11.5$  V

A series resistor in a charging circuit limits the current drawn from the external source.

The current will be extremely high in its absence. This is very dangerous.