

### Q. 03

**(a)** Six lead-acid type of secondary cells each of emf 2.0 V and internal resistance 0.015  $\Omega$  are joined in series to provide a supply to a resistance of 8.5  $\Omega$ . What are the current drawn from the supply and its terminal voltage?

**(b)** A secondary cell after long use has an emf of 1.9 V and a large internal resistance of 380  $\Omega$ . What maximum current can be drawn from the cell? Could the cell drive the starting motor of a car?

Answer

**(a)** Number of secondary cells,  $n = 6$

Emf of each secondary cell,  $E = 2.0$  V

Internal resistance of each cell,  $r = 0.015$   $\Omega$

series resistor is connected to the combination of cells.

Resistance of the resistor,  $R = 8.5$   $\Omega$

Current drawn from the supply =  $I$ , which is given by the relation,

$$I = \frac{nE}{R + nr}$$
$$= \frac{6 \times 2}{8.5 + 6 \times 0.015}$$

$$= \frac{12}{8.59} = 1.39 \text{ A}$$

Terminal voltage,  $V = IR = 1.39 \times 8.5 = 11.87 \text{ A}$

Therefore, the current drawn from the supply is 1.39 A and terminal voltage is 11.87 A.

**(b)** After a long use, emf of the secondary cell,  $E = 1.9 \text{ V}$

Internal resistance of the cell,  $r = 380 \Omega$

$$= \frac{E}{r} = \frac{1.9}{380} = 0.005 \text{ A}$$

Hence, maximum current

Therefore, the maximum current drawn from the cell is 0.005 A. Since a large current is required to start the motor of a car, the cell cannot be used to start a motor.